

# Experiment 7 - Week 1

- Week 1
  - Test the sequencer and able to increment PC.
  - Develop the RTL statements for the CPU instructions.  
(submit as post-lab)


# CPU Instruction (Fall 2025)


Instruction	Instruction code	Operation
NOP	00000000	No operation
LOADI R <sub>n</sub> ,X	0001000n X	$R_n \leftarrow X$
LOAD R <sub>n</sub> ,X	0010000n X	$R_n \leftarrow M[X]$
STORE X,R <sub>m</sub>	0011000m X	$M[X] \leftarrow R_m$
MOVE R <sub>n</sub> ,R <sub>m</sub>	0100000n	$R_n \leftarrow R_m, m \neq n$
ADD R <sub>n</sub> ,R <sub>m</sub>	0101000n	$R_n \leftarrow R_n + R_m, m \neq n$
SUB R <sub>n</sub> ,R <sub>m</sub>	0110000n	$R_n \leftarrow R_n - R_m, m \neq n$
TESTNZ R <sub>m</sub>	0111000m	$Z \leftarrow \text{not } V, V = \text{OR of the bits of } R_m$
TESTZ R <sub>m</sub>	1000000m	$Z \leftarrow V, V = \text{OR of the bits of } R_m$
JUMP X	10010000 X	$PC \leftarrow X$
JUMPZ X	10100000 X	If (Z = 1) then $PC \leftarrow X$
LOADSP X	10110000 X	$SP \leftarrow X$
PEEP R <sub>n</sub>	1100000n	$R_n \leftarrow M[SP]$
PUSH R <sub>n</sub>	1101000n	$M[--SP] \leftarrow R_n$ Pre-increment
POP R <sub>n</sub>	1110000n	$R_n \leftarrow M[SP++]$ Post-decrement
HALT	11110000	$PC \leftarrow 0$ , stop microsequencer

X = 8-bit data or  
address  
m, n = 0 or 1, m ≠ n
 
# Part 1A - Microsequencer

- Clock - system clock
- Enable - enables microsequencer
- Clear - reset the uPC register in the microsequencer to 0
- Opcode - 4-bit opcode
- Requires two clock cycle




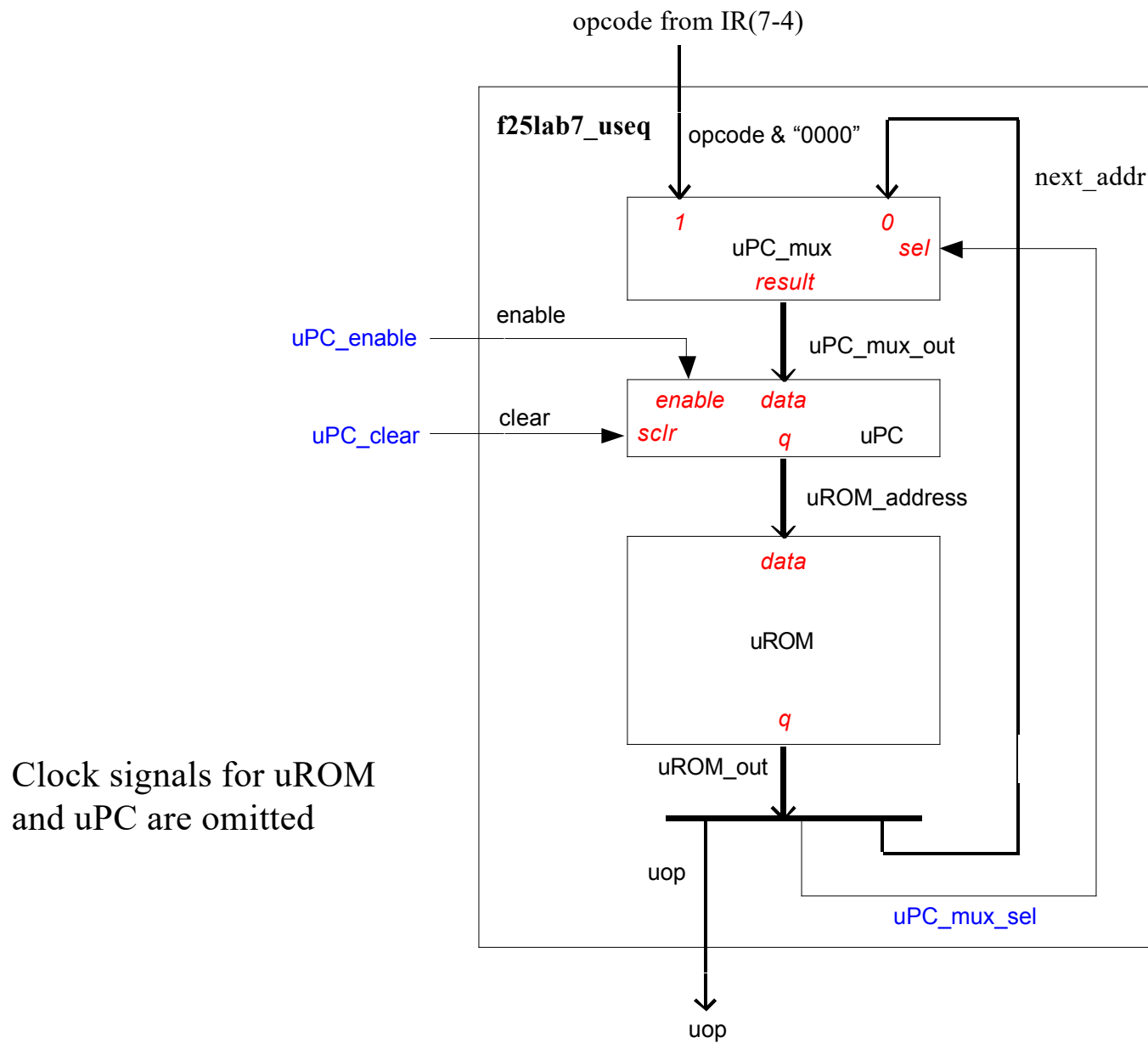

# Micro-ROM


- 256 words
- Width of each micro-ROM word is `uROM_width`
- `uROM_file` is the name of the mif with the content of the micro-ROM

# Micro-ROM format

 
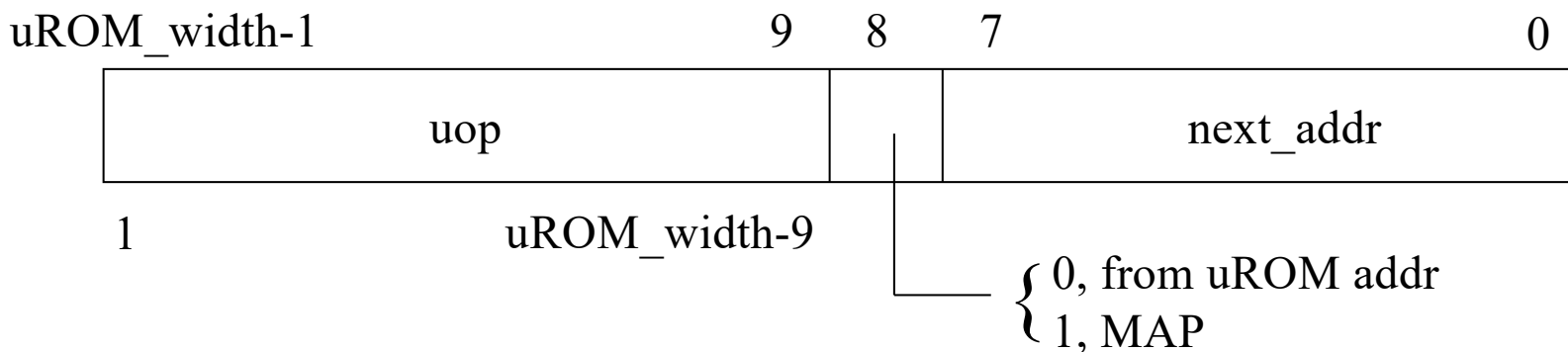
# Component Declaration

```
component f25lab7_useq
generic (uROM_width: integer;          -- uROM width
         uROM_file: string);          -- uROM file path
port (opcode: in std_logic_vector(3 downto 0);
      uop: out std_logic_vector(1 to (uROM_width-9));
      debug_map_addr: out std_logic_vector(8 downto 0);  -- for debugging
      enable, clear, clock: in std_logic);
end component;
```



# Part 1A – Test Microsequencer

Create a project for lab7 Part 1A with following code:

```
library ieee; use ieee.std_logic_1164.all;
library lpm; use lpm.lpm_components.all;
entity lab7Part1A is
port (clk, clear: in std_logic;
      useqEnOut: out std_logic;
      ctrlSignals: out std_logic_vector(0 to 7));
end lab7Part1A;
architecture structural of lab7Part1A is
```

```
-- add component declaration of f25lab7_useq
```

```
    signal useqEnable, useqClear: std_logic;
    signal uop: std_logic_vector(0 to 7);
```

```
begin
```

```
    delay: lpm_counter generic map(lpm_width=>2) port map(clock=>clk, cout=>useqEnable);
```

```
    useqClear <= clear;
```

```
    useqEnOut <= useqEnable;
```


```
    labelG: for i in 0 to 7 generate
```

```
        ctrlSignals(i) <= uop(i) and useqEnable;
```

```
    end generate;
```

```
-- add port map statement of f25lab7_useq, use the uROM Test file in the next slide
```

```
end structural;
```

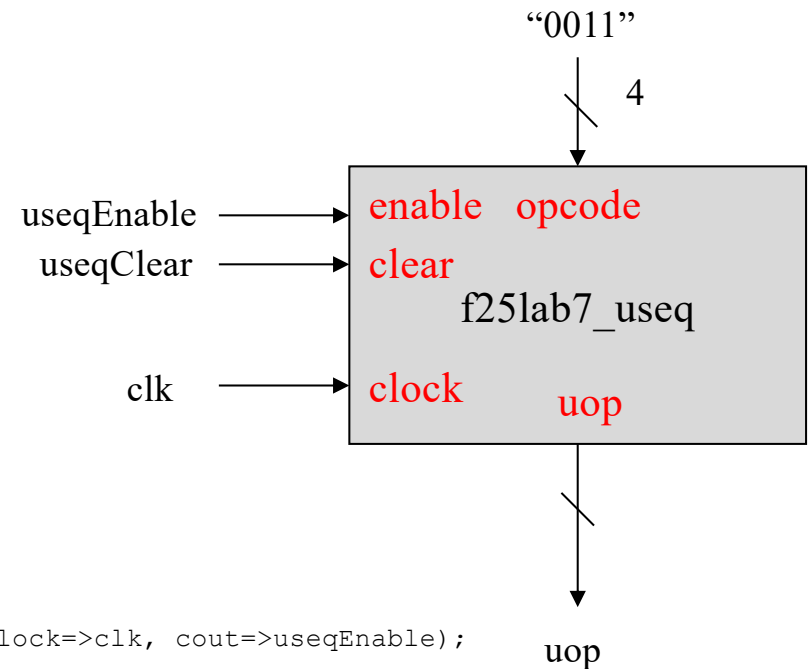



# Part 1A – uROM Test File

```
-- uROM Test File 1A
-- 8-bit control signals
```

```
WIDTH=17;
DEPTH=256;
ADDRESS_RADIX=HEX;
DATA_RADIX=BIN;
```

```
CONTENT BEGIN
```

```
  [0..FF]: 000000000000000000;
```

```
--      uop
```

```
--      01234567M01234567
```

```
00: 00000000000000001; -- control signal = 00000000, next address = 0x01
```

```
01: 00000001000000010; -- control signal = 00000001, next address = 0x02
```

```
02: 0000001000000011; -- control signal = 00000010, next address = 0x03
```

```
03: 0000001100000100; -- control signal = 00000011, next address = 0x04
```

```
04: 00000100100000000; -- control signal = 00000100, use MAP, go to address 0x30
```

```
30: 00000101000110001; -- control signal = 00000101, next address = 0x31
```

```
31: 00000110000110010; -- control signal = 00000110, next address = 0x32
```

```
32: 00000111000110011; -- control signal = 00000111, next address = 0x33
```

```
33: 00001000000000001; -- control signal = 00001000, next address = 0x01
```

```
END;
```


control signal

mux select

next address


- Assign
  - $\text{clk} = \text{key3}$ ,  $\text{clear} = \text{sw0}$ ,  $\text{useqEnOut} = \text{ledg7}$
  - $\text{ctrlSignals}(0) = \text{ledr7}$ ,  $\text{ctrlSignals}(1) = \text{ledr6}$ , ...,  $\text{ctrlSignals}(7) = \text{ledr0}$
- When  $\text{useqEnOut}$  goes high, you should see  $\text{ledr}(7-0) =$ 
  - “00000000”,
  - “00000001”, “00000010”, “00000011”, “00000100”
  - “00000101”, “00000110”, “00000111”, “00001000”

repeat

 
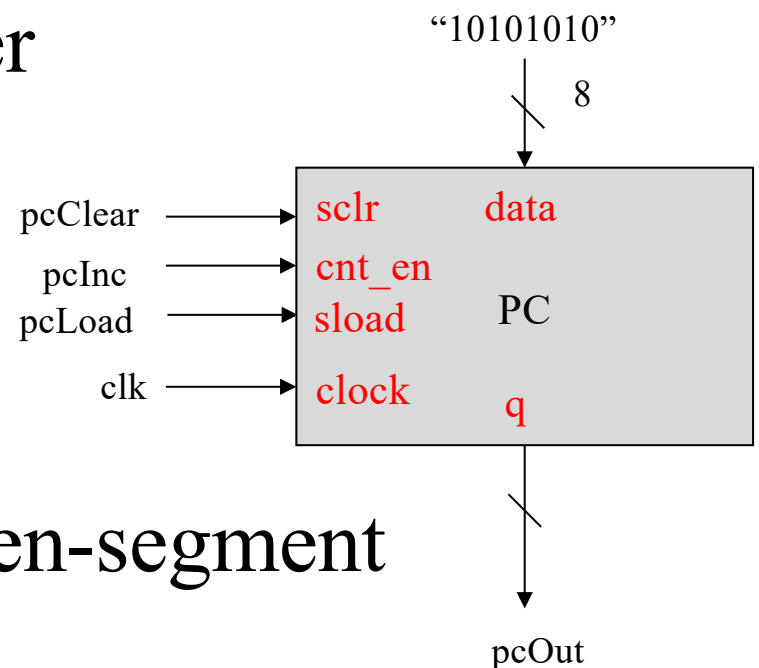
## Part 1B -Use Microsequencer to clear, load and increment PC

- Add PC using lpm\_counter
- Use uop(0) as pcInc
- Use uop(1) as pcLoad
- Use uop(2) as pcClear
- Display PC using two seven-segment displays



# Part 1B

Create a project for lab7 Part 1B with following code:

```
library ieee; use ieee.std_logic_1164.all;
library lpm; use lpm.lpm_components.all;
entity lab7Part1B is
port (clk, clear: in std_logic;
      useqEnOut: out std_logic;
      pcSeg1, pcSeg2: out std_logic_vector(0 to 6);
      ctrlSignals: out std_logic_vector(0 to 7));
end lab7Part1B;
architecture structural of lab7Part1B is


-- add component declaration of f25lab7_useq
-- add component declaration for seven-segment decoder

    signal useqEnable, useqClear: std_logic;
    signal uop: std_logic_vector(0 to 7);
    signal pcInc, pcLoad, pcClear: std_logic;

begin
    delay: lpm_counter generic map(lpm_width=>2) port map(clock=>clk, cout=>useqEnable);
    useqClear <= clear;
    useqEnOut <= useqEnable;
    labelG: for i in 0 to 7 generate
        ctrlSignals(i) <= uop(i) and useqEnable;
    end generate;
    pcInc <= uop(0) and useqEnable;
    pcLoad <= uop(1) and useqEnable;
    pcClear <= uop(2) and useqEnable;

    -- add port map statement of f25lab7_useq, use the uROM Test file in the next slide
    -- add pc register, seven-segment display

end structural;
```

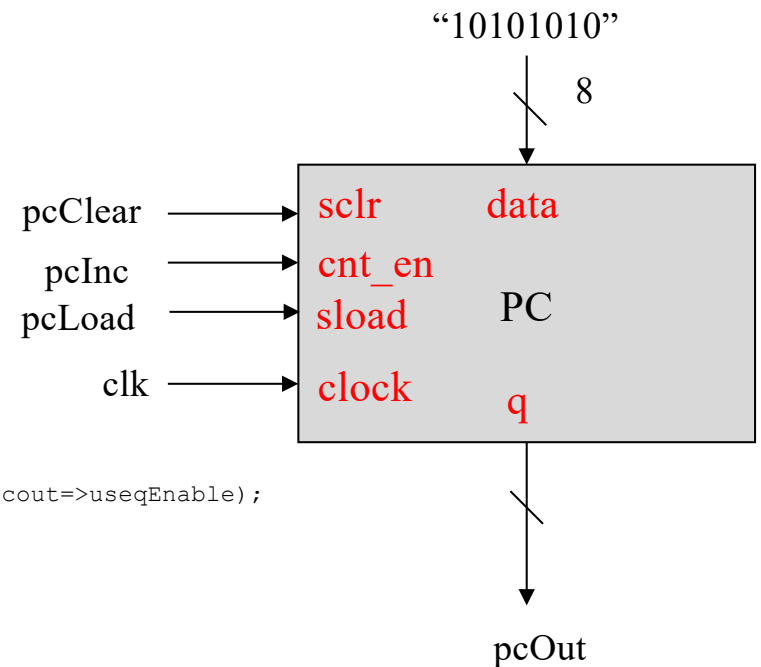

# Part 1B – uROM Test File

```
-- uROM Test File 1B
-- 8-bit control signals
```

```
WIDTH=17;
DEPTH=256;
ADDRESS_RADIX=HEX;
DATA_RADIX=BIN;
```

```
CONTENT BEGIN
```

```
  [0..FF]: 000000000000000000;
```

```
--      uop
```

```
--      01234567M01234567
```

```
00: 00000000000000001; -- control signal = 00000000, next address = 0x01
```

```
01: 00100001000000010; -- control signal = 00100001, next address = 0x02, clear PC, PC = 0x00
```

```
02: 1000001000000011; -- control signal = 10000010, next address = 0x03, inc PC, PC = 0x01
```

```
03: 10000011000000100; -- control signal = 10000011, next address = 0x04, inc PC, PC = 0x02
```

```
04: 00000100100000000; -- control signal = 00000100, use MAP, go to address 0x30
```

```
30: 01000101000110001; -- control signal = 01000101, next address = 0x31, load PC, PC = 0xAA
```

```
31: 00000110000110010; -- control signal = 00000110, next address = 0x32
```

```
32: 10000111000110011; -- control signal = 10000111, next address = 0x33, inc PC, PC = 0xAB
```

```
33: 00001000000000001; -- control signal = 00001000, next address = 0x01,
```

```
END;
```

control signal

mux select

next address

# Part 1B – uROM Test File

```
-- uROM Test File 1B
-- 8-bit control signals
```

```
WIDTH=17;
DEPTH=256;
ADDRESS_RADIX=HEX;
DATA_RADIX=BIN;
```

```
CONTENT BEGIN
```

```
  [0..FF]: 000000000000000000;
```

```
--      uop
```

```
--      01234567M01234567
```

```
00: 00000000 00000001; -- control signal = 00000000, next address = 0x01
```

```
01: 00100001 00000010; -- control signal = 00100001, next address = 0x02, clear PC, PC = 0x00
```

```
02: 10000010 00000011; -- control signal = 10000010, next address = 0x03, inc PC, PC = 0x01
```

```
03: 10000011 00000100; -- control signal = 10000011, next address = 0x04, inc PC, PC = 0x02
```

```
04: 00000100 00000000; -- control signal = 00000100, use MAP, go to address 0x30
```

```
30: 01000101 00011001; -- control signal = 01000101, next address = 0x31, load PC, PC = 0xAA
```


```
31: 00000110 00011001; -- control signal = 00000110, next address = 0x32
```

```
32: 10000111 00011001; -- control signal = 10000111, next address = 0x33, inc PC, PC = 0xAB
```


```
33: 00001000 00000001; -- control signal = 00001000, next address = 0x01,
```

```
END;
```

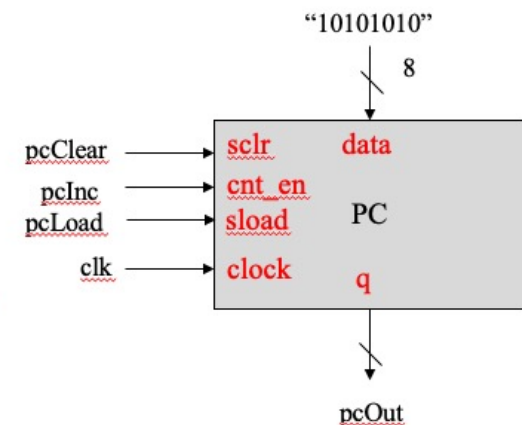- uop(0) = pcInc
- uop(1) = pcLoad
- uop(2) = pcClear



 - Assign
  - $\text{clk} = \text{key3}$ ,  $\text{clear} = \text{sw0}$ ,  $\text{useqEnOut} = \text{ledg7}$
  - $\text{ctrlSignals}(0) = \text{ledr7}$ ,  $\text{ctrlSignals}(1) = \text{ledr6}$ , ...,  $\text{ctrlSignals}(7) = \text{ledr0}$
  - $\text{pcSeg1} = \text{hex0}$ ,  $\text{pcSeg2} = \text{hex1}$
- You should see  
 $\text{pcSeg2}, \text{pcSeg1} = 0x00, 0x01, 0x02, 0xAA, 0xAB, \dots$



# Assignments

- Week 1
  - Test the sequencer and able to increment PC.
  - Develop the RTL statements for the CPU instructions.  
(submit as post-lab)