

ECE 495

Computer Engineering Design Laboratory

Lab 7

Microprogrammed CPU Design

Group 302

Bryan Galecio
Kevin Galarraga

December 11, 2025

On my honor, I pledge that I have not violated the provisions of the NJIT Academic Honor Code.



Kevin Galarraga

	Grade
Demo: 11/20 Part 1 A, B OK 11/23 Part 2 OK Verified: OK #1-6 all OK Report:	

OBJECTIVE AND INTRODUCTION

The primary objective of this effort is to implement a microprogrammed CPU design on an FPGA using VHDL, the Library of Parameterized Modules (LPM), and structural modeling techniques. **Figure 1** shows a high-level block diagram illustrating how the FPGA will be used to realize the microprogrammed CPU.

 


Figure 1: High-level block diagram showing how the CPU connects to an I/O device (display), and how the address and data lines interface with RAM, unidirectionally for the address bus and bidirectionally for the data bus, to fetch program instructions.

Processor control units can be designed in several ways, such as through hardwired control logic. However, a microprogrammed control unit offers significantly greater flexibility, easier debugging, simpler modification, and reduced design complexity. By storing control information in memory rather than embedding it in fixed hardware, a microprogrammed CPU enables a cleaner flow of control signals and is generally more adaptable to changes or additions in the instruction set.

The Library of Parameterized Modules provides the essential building blocks for the CPU design, including Read-Only Memory (ROM), Random-Access Memory (RAM), D flip-flops, Multiplexers, ALUs, and Counters. Because these modules are parameterized, their behavior and size can be adjusted during instantiation. This allows us to customize data widths, enable or disable optional features, and tailor each component to the specific needs of our architecture.

At the core of the microprogrammed design is the microsequencer, a component not included in the LPM library. Thus, before implementing the full CPU, we first designed a functional microsequencer capable of supplying the CPU with programmed control signals. **Figure 2** shows the block diagram of the microsequencer. The instruction register provides the opcode to the microsequencer, which uses this opcode, along with mapping bits, to access the starting address of the instruction's micro-operation in the ROM. From there, the microsequencer advances through consecutive micro-operations until the instruction is complete. **Figure 3** illustrates the ROM output format used by the microsequencer. Because the address line is 8 bits wide, the ROM contains 2^8 address locations. Each ROM word encodes the CPU control signals, a mapping bit, and the next address (from MSB to LSB), with the specific arrangement determined by the CPU design.

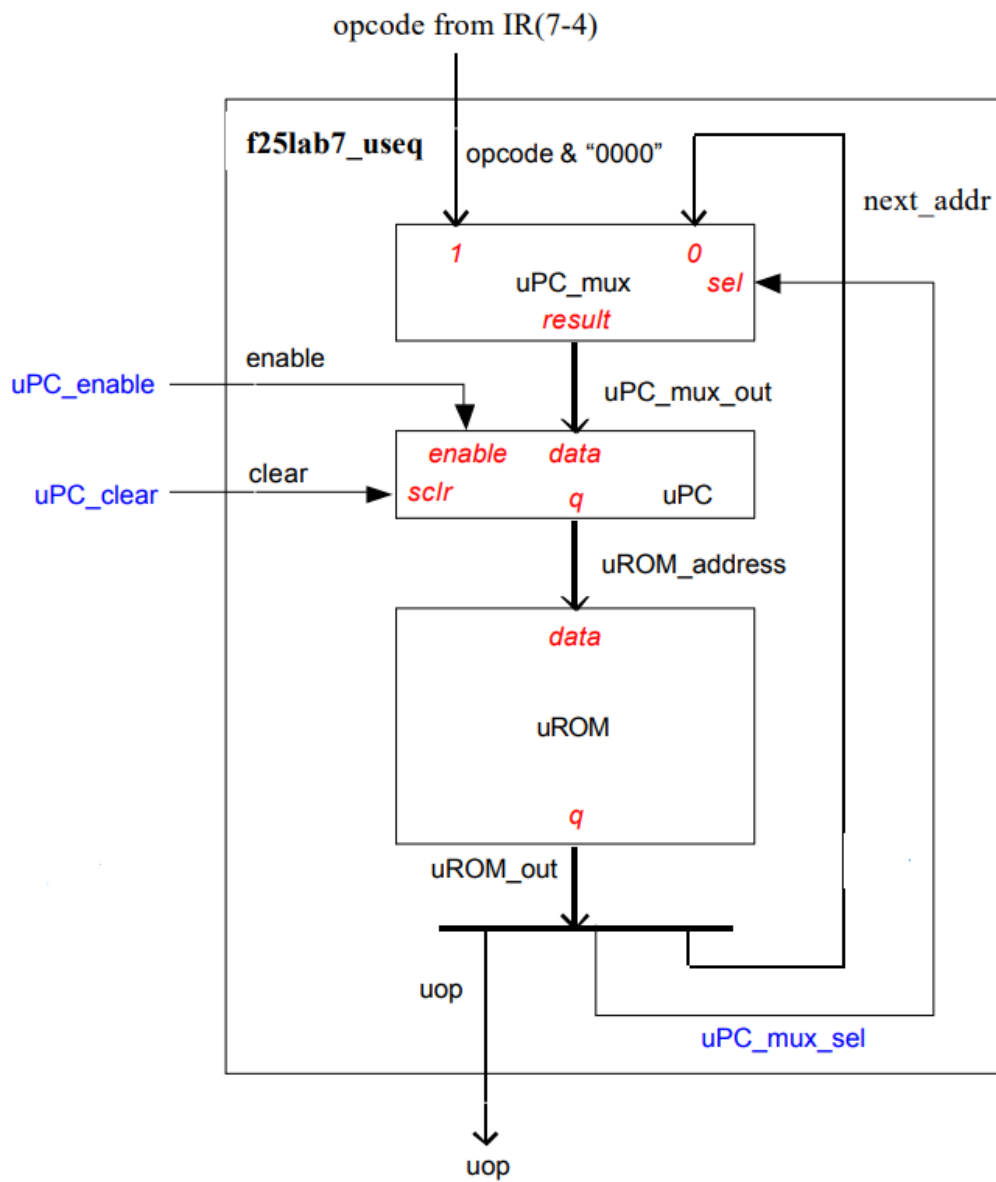


Figure 2: Block diagram of the microsequencer.

 


Figure 3: ROM output format used by the microsequencer.

With the microsequencer defined, we then needed a memory system capable of holding the program instructions. For this lab, we implemented a RAM block that includes address and data registers. This RAM stores the sequence of instructions that the CPU will execute during its fetch and execute cycles. The contents of RAM must adhere to the instruction set architecture (ISA) defined in **Figure 4**, which lists each instruction, its opcode, and its intended operation. **Figure 5** provides a block diagram of the RAM subsystem.

Instruction	Instruction code	Operation
NOP	00000000	No operation
LOADI R _n ,X	0001000n X	$R_n \leftarrow X$
LOAD R _n ,X	0010000n X	$R_n \leftarrow M[X]$
STORE X,R _m	0011000m X	$M[X] \leftarrow R_m$
MOVE R _n ,R _m	0100000n	$R_n \leftarrow R_m, m \neq n$
ADD R _n ,R _m	0101000n	$R_n \leftarrow R_n + R_m, m \neq n$
SUB R _n ,R _m	0110000n	$R_n \leftarrow R_n - R_m, m \neq n$
TESTNZ R _m	0111000m	$Z \leftarrow \text{not } V, V = \text{OR of the bits of } R_m$
TESTZ R _m	1000000m	$Z \leftarrow V, V = \text{OR of the bits of } R_m$
JUMP X	10010000 X	$PC \leftarrow X$
JUMPZ X	10100000 X	If ($Z = 1$) then $PC \leftarrow X$
LOADSP X	10110000 X	$SP \leftarrow X$
PEEP R _n	1100000n	$R_n \leftarrow M[SP]$
PUSH R _n	1101000n	$M[--SP] \leftarrow R_n$ Pre-increment
POP R _n	1110000n	$R_n \leftarrow M[SP++]$ Post-decrement
HALT	11110000	$PC \leftarrow 0$, stop microsequencer

Figure 4: Instruction set table showing the 16 CPU instructions, their instruction codes, and their corresponding operations.

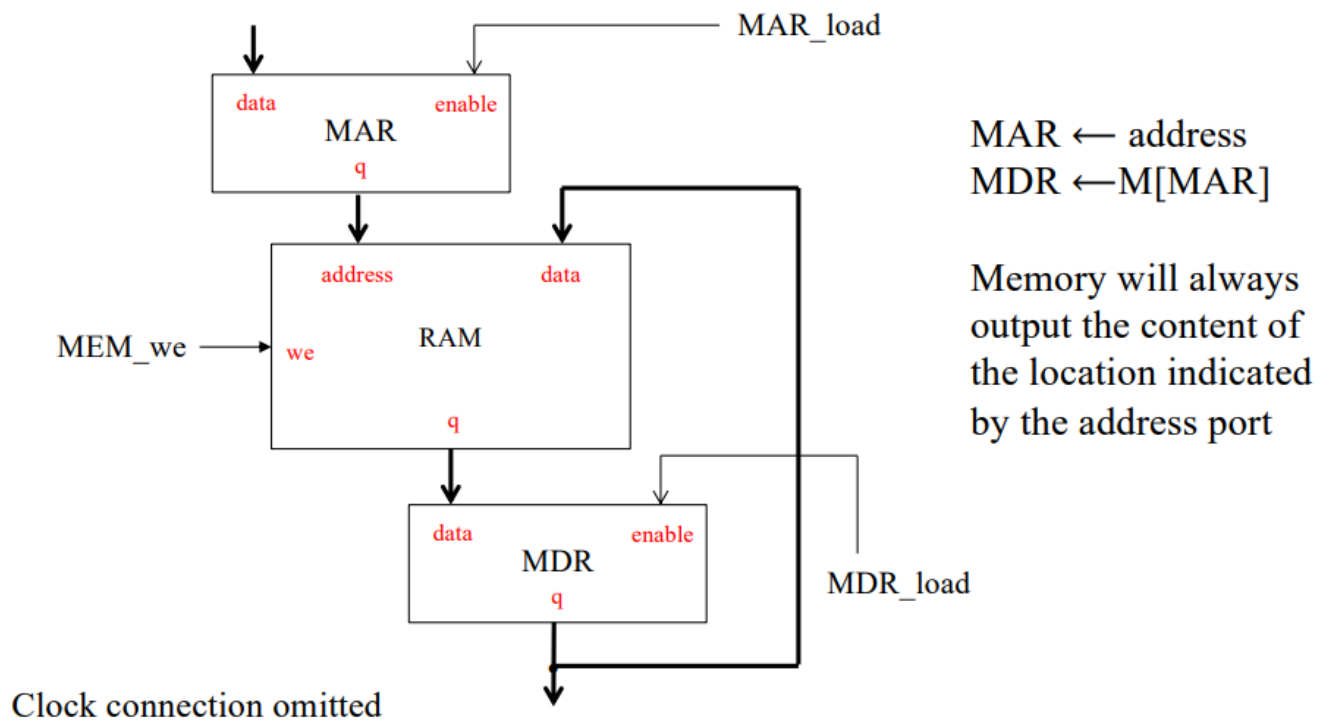


Figure 5: Block diagram of the RAM subsystem and its connections.

Having established the foundational components, we next considered how binary control signals (1s and 0s) orchestrate CPU behavior during instruction execution. Each instruction consists of a sequence of micro-operations that are activated by specific control signals. To determine these control signals and their order, we rely on Register Transfer Language (RTL). RTL provides a clear abstraction of the data transfers and operations that occur in each cycle of an instruction, and serves as the most direct guide for generating the corresponding microinstructions.

With the hardware requirements, microsequencer design, ISA definition, and RTL descriptions in place, we are prepared to develop the complete microprogrammed CPU. The design, RTL code, and memory structures will be implemented in VHDL and synthesized onto the *Altera Cyclone® IV EP4CE115F29C7* FPGA using *Intel® Quartus® II*.

THEORY AND METHODS

Based on the microsequencer block diagram shown in **Figure 2**, we designed a VHDL program that synthesizes its functionality using components from the Library of Parameterized Modules (LPM), including multiplexers, D flip-flops, and ROM. The micro-operation (UOP) size was set to the ROM output size minus 9, since 8 bits encode the next address and 1 bit represents the internal mapping signal. The resulting VHDL program is parametrized, allowing it to be instantiated as a reusable component for the microprogrammed CPU design, as shown in **Figure 6**.

```
library ieee;
use ieee.std_logic_1164.all;
library lpm;
use lpm.lpm_components.all;

entity uSequencer is
  generic(
    uROM_width: integer := 10;
    uROM_file: string := ""
  );
  port(
    opcode: in std_logic_vector(3 downto 0);
    uop: out std_logic_vector(1 to (uROM_width-9));
    debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging
    enable, clear: in std_logic;
    clock: in std_logic
  );
end uSequencer;

architecture structural of uSequencer is
  signal uROM_address: std_logic_vector (7 downto 0);
```

```

signal uROM_out: std_logic_vector (uROM_width-1 downto 0);
signal uPC_mux_data: std_logic_2D(1 downto 0, 7 downto 0);
signal uPC_mux_sel: std_logic_vector(0 to 0);
signal uPC_mux_out: std_logic_vector(7 downto 0);
signal temp: std_logic_vector(7 downto 0);

begin
    temp <= opcode & "0000";

    for_label: for i in 0 to 7 generate
        uPC_mux_data(0, i) <= uROM_out(i);
        uPC_mux_data(1, i) <= temp(i);
    end generate;

    uPC_mux_sel(0) <= uROM_out(8);

    uPC_mux: lpm_mux
        generic map (lpm_width=>8, lpm_size=>2, lpm_widths=>1)
        port map (result=>uPC_mux_out, data=>uPC_mux_data, sel=>uPC_mux_sel);
    uPC: lpm_ff
        generic map (lpm_width=>8)
        port map (clock=>clock, data=>uPC_mux_out, q=>uROM_address, sclr=>clear,
enable=>enable);
    uROM: lpm_rom
        generic map (lpm_widthad=>8, lpm_width=>uROM_width, lpm_file=>uROM_file)
        port map (address=>uROM_address, q=>uROM_out, inclock=>clock,
outclock=>clock);

    uop <= uROM_out(uROM_width-1 downto 9);
    debug_map_addr <= uROM_out(8 downto 0);

```



```
end structural;
```

Figure 6: Parameterized VHDL program of the microsequencer.

To verify the microsequencer, we tested it in two separate VHDL programs (**Figures 7 and 8**). Because an instruction register was not yet implemented, we hardwired the opcode 0011 and used a memory initialization file (.mif) in *Intel Quartus® II* to load the ROM. In the program of **Figure 7**, a counter enables the microsequencer every four clock pulses, advancing through addresses until the mapping signal is set high. The ROM then transitions to address “00110000” (0x30 in hex or 48 in decimal), where the microsequencer continues until cleared, as the mapping signal is no longer declared.

In **Figure 8**, we added a register representing the CPU’s memory address reference point. This setup tests the microsequencer’s ability to correctly set control signals in conjunction with a pseudo instruction. The corresponding .mif files for these tests are shown in **Figures 9 and 10**. At address 0x30, control signals are activated to load and increment the program counter (PC), which we confirmed using a seven-segment display component developed in previous labs.

```
library ieee;
use ieee.std_logic_1164.all;
library lpm;
use lpm.lpm_components.all;

entity test_uSequencer is
    port(
        button, clear: in std_logic;
        useqEnOut: out std_logic;
        ctrlSignals: out std_logic_vector(0 to 7);
        M_disp, disp1, disp0: out std_logic_vector(0 to 6)
```

```

    );
end test_uSequencer;

architecture structural of test_uSequencer is
    component uSequencer is
        generic(
            uROM_width: integer := 10;
            uROM_file: string := ""
        );
        port(
            opcode: in std_logic_vector(3 downto 0);
            uop: out std_logic_vector(1 to (uROM_width-9));
            debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging
            enable, clear: in std_logic;
            clock: in std_logic
        );
    end component;

    component seven_segment_display is
        port(
            digit: in std_logic_vector(3 downto 0);
            display: out std_logic_vector(0 to 6)
        );
    end component;

    signal useqEnable, useqClear, clk: std_logic;
    signal uop: std_logic_vector(0 to 7);
    signal address_out: std_logic_vector(8 downto 0);
    signal M, addr_hex1, addr_hex0: std_logic_vector(3 downto 0);
begin

```

```

    clk <= not(button);

    delay: lpm_counter generic map(lpm_width=>2) port map(clock=>clk,
cout=>useqEnable);

    useqClear <= clear;
    useqEnOut <= useqEnable;

    labelG: for i in 0 to 7 generate
        ctrlSignals(i) <= uop(i) and useqEnable;
    end generate;

    uSeq: uSequencer
        generic map(uROM_width=>17, uROM_file=>"test_uSequencer_file.mif")
        port map(opcode=>"0011", uop=>uop, debug_map_addr=>address_out,
enable=>useqEnable, clear=>useqClear, clock=>clk);

    M <= "000" & address_out(8);
    addr_hex1 <= address_out(7 downto 4);
    addr_hex0 <= address_out(3 downto 0);
    display1: seven_segment_display port map(digit=>M, display=>M_disp);
    display2: seven_segment_display port map(digit=>addr_hex1, display=>disp1);
    display3: seven_segment_display port map(digit=>addr_hex0, display=>disp0);
end structural;

```

Figure 7: VHDL test program for the microsequencer using a counter and hardwired opcode.

```

library ieee;
use ieee.std_logic_1164.all;

```

```

library lpm;
use lpm.lpm_components.all;

entity test_uSequencer_PC is
    port(
        button, clear: in std_logic;
        useqEnOut: out std_logic;
        ctrlSignals: out std_logic_vector(0 to 7);
        pc_Seg1, pc_Seg0, M_disp, disp1, disp0: out std_logic_vector(0 to 6)
    );
end test_uSequencer_PC;

architecture structural of test_uSequencer_PC is
    component uSequencer is
        generic(
            uROM_width: integer := 10;
            uROM_file: string := ""
        );
        port(
            opcode: in std_logic_vector(3 downto 0);
            uop: out std_logic_vector(1 to (uROM_width-9));
            debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging
            enable, clear: in std_logic;
            clock: in std_logic
        );
    end component;

    component seven_segment_display is
        port(
            digit: in std_logic_vector(3 downto 0);

```

```

        display: out std_logic_vector(0 to 6)
    );
end component;

signal useqEnable, useqClear, clk: std_logic;
signal pcInc, pcLoad, pcClear: std_logic;
signal pcOut: std_logic_vector(7 downto 0);
signal uop: std_logic_vector(0 to 7);
signal address_out: std_logic_vector(8 downto 0);
signal M, addr_hex1, addr_hex0, pc_hex1, pc_hex0: std_logic_vector(3 downto 0);
begin
    clk <= not(button);
    delay: lpm_counter
        generic map(lpm_width=>2)
        port map(clock=>clk, cout=>useqEnable);

    useqClear <= clear;
    useqEnOut <= useqEnable;

    labelG: for i in 0 to 7 generate
        ctrlSignals(i) <= uop(i) and useqEnable;
    end generate;

    pcInc <= uop(0) and useqEnable;
    pcLoad <= uop(1) and useqEnable;
    pcClear <= uop(2) and useqEnable;

    uSeq: uSequencer
        generic map(uROM_width=>17,
uROM_file=>"test_uSequencer_PC_file.mif")

```

```

        port map(opcode=>"0011", uop=>uop, debug_map_addr=>address_out,
enable=>useqEnable, clear=>useqClear, clock=>clk);

pc: lpm_counter
    generic map(lpm_width=>8)
    port map(sload=>pcLoad, data=> "10101010", q=>pcOut, cnt_en=>pcInc,
sclr=>pcClear, clock=>clk);

M <= "000" & address_out(8);
addr_hex1 <= address_out(7 downto 4);
addr_hex0 <= address_out(3 downto 0);
pc_hex1 <= pcOut(7 downto 4);
pc_hex0 <= pcOut(3 downto 0);
display1: seven_segment_display port map(digit=>M, display=>M_disp);
display2: seven_segment_display port map(digit=>addr_hex1, display=>disp1);
display3: seven_segment_display port map(digit=>addr_hex0, display=>disp0);
display4: seven_segment_display port map(digit=>pc_hex1, display=>pc_Seg1);
display5: seven_segment_display port map(digit=>pc_hex0, display=>pc_Seg0);

end structural;

```

Figure 8: VHDL test program for the microsequencer, including a pseudo instruction register.

```

1  -- uROM Test File
2  -- 8-bit control signals
3  WIDTH=17;
4  DEPTH=256;
5  ADDRESS_RADIX=HEX;
6  DATA_RADIX=BIN;
7  CONTENT BEGIN
8    [0..FF]: 000000000000000000;
9  -- uop
10 -- 01234567M01234567
11 00: 000000000000000001; -- control signal = 00000000, next address = 0x01
12 01: 000000010000000010; -- control signal = 00000001, next address = 0x02
13 02: 000000100000000011; -- control signal = 00000010, next address = 0x03
14 03: 000000110000000100; -- control signal = 00000011, next address = 0x04
15 04: 000001001000000000; -- control signal = 00000100, use MAP, go to address 0x30
16 30: 00000101000110001; -- control signal = 00000101, next address = 0x31
17 31: 00000110000110010; -- control signal = 00000110, next address = 0x32
18 32: 00000111000110011; -- control signal = 00000111, next address = 0x33
19 33: 000010000000000001; -- control signal = 00001000, next address = 0x01
20 END;

```

Figure 9: Memory initialization file (.mif) for the microsequencer test in **Figure 7**.

```

1  -- uROM Test File
2  -- 8-bit control signals
3  WIDTH=17;
4  DEPTH=256;
5  ADDRESS_RADIX=HEX;
6  DATA_RADIX=BIN;
7  CONTENT BEGIN
8    [0..FF]: 000000000000000000;
9  -- uop
10 -- 01234567M01234567
11 00: 000000000000000001; -- control signal = 00000000, next address = 0x01
12 01: 001000010000000010; -- control signal = 00100001, next address = 0x02, clear PC, PC = 0x00
13 02: 100000100000000011; -- control signal = 10000010, next address = 0x03, inc PC, PC = 0x01
14 03: 100000110000000100; -- control signal = 10000011, next address = 0x04, inc PC, PC = 0x02
15 04: 000001001000000000; -- control signal = 00000100, use MAP, go to address 0x30
16 30: 01000101000110001; -- control signal = 01000101, next address = 0x31, load PC, PC = 0xAA
17 31: 00000110000110010; -- control signal = 00000110, next address = 0x32
18 32: 10000111000110011; -- control signal = 10000111, next address = 0x33, inc PC, PC = 0xAB
19 33: 000010000000000001; -- control signal = 00001000, next address = 0x01,
20 END;

```

Figure 10: Memory initialization file (.mif) for the microsequencer test in **Figure 8**.

In addition to the microsequencer, the RAM subsystem is a critical component for instruction storage and execution. **Figure 11** shows the VHDL implementation of the RAM subsystem. We tested the RAM using initialized ROM and RAM .mif files: the ROM .mif provided control signals to load the MAR and MDR registers, while the RAM .mif verified data at specific address locations. These .mif files are illustrated in **Figure 12**.

```

library ieee;
use ieee.std_logic_1164.all;

library lpm;
use lpm.lpm_components.all;

entity test_ram is
    port(
        button, clear: in std_logic;
        useqEnOut: out std_logic;
        marData: in std_logic_vector(7 downto 0); -- connected to switches, input
to MAR
        marSegHi, marSegLo, mdrSegHi, mdrSegLo, nextAddrHi, nextAddrLo: out
std_logic_vector(0 to 6);
        ctrlSignals: out std_logic_vector(0 to 7)
    );
end test_ram;

architecture structural of test_ram is
    component uSequencer is
        generic(
            uROM_width: integer := 10;
            uROM_file: string := ""
        );
        port(
            opcode: in std_logic_vector(3 downto 0);
            uop: out std_logic_vector(1 to (uROM_width-9));
            debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging
            enable, clear: in std_logic;
            clock: in std_logic

```



```

);
end component;

component seven_segment_display is
    port(
        digit: in std_logic_vector(3 downto 0);
        display: out std_logic_vector(0 to 6)
    );
end component;

signal clk, useqEnable, useqClear, marLoad, mdrLoad, memWE: std_logic;
signal uop: std_logic_vector(0 to 7);
signal marADig, marBDig, mdrADig, mdrBDig, nextAADig, nextABDig: std_logic_vector(3
downto 0);
signal marOut, memOut, mdrOut: std_logic_vector(7 downto 0);
signal address_out: std_logic_vector(8 downto 0);
begin
    clk <= not(button);
    useqClear <= clear;
    useqEnOut <= useqEnable;
    marLoad <= uop(0) and useqEnable;
    mdrLoad <= uop(1) and useqEnable;
    memWE <= uop(2) and useqEnable;

    marADig <= marOut(7 downto 4);
    marBDig <= marOut(3 downto 0);
    mdrADig <= mdrOut(7 downto 4);
    mdrBDig <= mdrOut(3 downto 0);
    nextAADig <= address_out(7 downto 4);
    nextABDig <= address_out(3 downto 0);

```

```

labelG: for i in 0 to 7 generate
    ctrlSignals(i) <= uop(i) and useqEnable;
end generate;

delay: lpm_counter generic map(lpm_width=>2) port map(clock=>clk,
cout=>useqEnable);

microSequencer: uSequencer
    generic map(uROM_width=>17, uROM_file=>"test_rom_file.mif")
    port map(opcode=>"0000", uop=>uop, debug_map_addr=>address_out,
enable=>useqEnable, clear=>useqClear, clock=>clk);

marReg: lpm_ff
    generic map(lpm_width=>8)
    port map(data=>marData, q=>marOut, clock=>clk, enable=>marLoad);

mdrReg: lpm_ff
    generic map(lpm_width=>8)
    port map(data=>memOut, q=>mdrOut, clock=>clk, enable=>mdrLoad);

ram: lpm_ram_dq
    generic map(lpm_widthad=>8, lpm_width=>8,
lpm_file=>"test_ram_file.mif")
    port map(data=>mdrOut, address=>marOut, q=>memOut, inclock=>clk,
outclock=>clk, we=>memWE);

marA: seven_segment_display port map(digit=>marADig, display=>marSegHi);
marB: seven_segment_display port map(digit=>marBDig, display=>marSegLo);
mdrA: seven_segment_display port map(digit=>mdrADig, display=>mdrSegHi);
mdrB: seven_segment_display port map(digit=>mdrBDig, display=>mdrSegLo);
nextAddressA: seven_segment_display port map(digit=>nextAADig,
display=>nextAddrHi);
nextAddressB: seven_segment_display port map(digit=>nextABDig,
display=>nextAddrLo);

```

```
end structural;
```

Figure 11: VHDL implementation of the RAM subsystem and its connections.

```
1  -- uROM Test File
2  -- 8-bit control signals
3
4  WIDTH=17;
5  DEPTH=256;
6  ADDRESS_RADIX=HEX;
7  DATA_RADIX=BIN;
8
9  CONTENT BEGIN
10     [0..FF]: 000000000000000000;
11     --      uop
12     --      01234567M01234567
13     00: 000000000000000001; -- control signal (cs) = 00000000, next address (na) = 0x01
14     01: 100000010000000010; -- cs = 10000001, na = 0x02, Load MAR from sw, MAR = 0x54
15     02: 010000100000000011; -- cs = 01000010, na = 0x03, MDR <- M[MAR], MDR = 0xFC
16     03: 100000110000000100; -- cs = 10000011, na = 0x04, Load MAR from sw, MAR = 0x55
17     04: 010001000000000101; -- cs = 01000100, na = 0x05, MDR <- M[MAR], MDR = 0xDD
18     05: 100001010000000110; -- cs = 10000101, na = 0x06, Load MAR from sw, MAR = 0x56
19     06: 001001100000000111; -- cs = 00100110, na = 0x07, M[MAR] <- MDR
20     07: 100001110000001000; -- cs = 10000111, na = 0x08, Load MAR from sw, MAR = 0x54
21     08: 010010000000001001; -- cs = 01001000, na = 0x09, MDR <- M[MAR], MDR = 0xFC
22     09: 100010010000001010; -- cs = 10001001, na = 0x0A, Load MAR from sw, MAR = 0x56
23     0A: 010010100000000000; -- cs = 01001010, na = 0x00, MDR <- M[MAR], MDR = 0xDD
24 END;
```

```
1  -- RAM Test File
2
3  WIDTH=8;
4  DEPTH=256;
5  ADDRESS_RADIX=HEX;
6  DATA_RADIX=HEX;
7
8  CONTENT BEGIN
9      [0..FF]: 0;
10      54: FC;
11      55: DD;
12      56: AA;
13 END;
```

Figure 12: .mif files for testing RAM and microsequencer interactions.

Once the basic register, microsequencer, and RAM subsystems were implemented, we developed Register Transfer Level (RTL) statements for each CPU instruction. These RTL

statements guided the construction of a full CPU block diagram and the creation of a ROM file containing the micro-operations for each instruction. **Figures 13, 14, and 15** show the RTL statements, the CPU block diagram, and the ROM .mif file exported from a spreadsheet, respectively, ensuring consistency with the RTL logic.

```
# Develop the RTL statements for the CPU instructions:
```

```
# All instructions do Instruction Fetch:
```

```
F1: MAR ← PC # Load address of instruction
```

```
F2: MDR ← M[MAR], PC ← PC + 1 # Fetch instruction and increment PC
```

```
F3: IR ← MDR # Decode instruction
```

```
nop                00000000
```

```
- None -
```

```
loadi Rn, X        0001000n X
```

```
L11: MAR ← PC # Load memory address of immediate operand
```

```
L12: MDR ← M[MAR], PC ← PC + 1 # Fetch immediate operand and increment PC
```

```
L13: R0 ← MDR if IR(0) = 0, R1 ← MDR if IR(0) = 1 # Load immediate value into R0 if  
IR(0) = 0 else if IR(0) = 1 into R1
```

```
load Rn, X         0010000n X
```

```
L1: MAR ← PC # Load memory address of operand
```

```
L2: MDR ← M[MAR], PC ← PC + 1 # Fetch operand address and increment PC
```

```
L3: MAR ← MDR # Load effective address
```

```
L4: MDR ← M[MAR] # Fetch data from memory
```

```
L5: R0 ← MDR if IR(0) = 0, R1 ← MDR if IR(0) = 1 # Load data into R0 if IR(0) = 0 else if  
IR(0) = 1 load into R1
```

```
store X, Rn        0011000n X
```

ST1: MAR \leftarrow PC # Load memory address of operand

ST2: MDR \leftarrow M[MAR], PC \leftarrow PC + 1 # Fetch operand address and increment PC

ST3: MAR \leftarrow MDR # Load effective address

ST4: MDR \leftarrow R0 if IR(0) = 0, MDR \leftarrow R1 if IR(0) = 1 # Load data from R0 if IR(0) = 0 else if IR(0) = 1 load from R1

ST5: M[MAR] \leftarrow MDR # Store data into memory

move Rn, Rm 0100000n m!=n

M1: R0 \leftarrow R1 if IR(0) = 0, R1 \leftarrow R0 if IR(0) = 1 # Move value from R1 to R0 if IR(0) = 0 else if IR(0) = 1 move from R0 to R1

add Rn, Rm 0101000n m!=n

A1: R0 \leftarrow R0 + R1 if IR(0) = 0, R1 \leftarrow R0 + R1 if IR(0) = 1 # R0 plus R1 if IR(0) = 0 else if IR(0) = 1 R1 plus R0

sub Rn, Rm 0110000n m!=n

S1: R0 \leftarrow R0 - R1 if IR(0) = 0, R1 \leftarrow R1 - R0 if IR(0) = 1 # R0 minus R1 if IR(0) = 0 else if IR(0) = 1 R1 minus R0

testnz Rn 0111000n

TN1: Z \leftarrow NOT(R0(0) OR ... OR R0(7)) if IR(0) = 0, \leftarrow NOT(R1(0) OR ... OR R1(7)) if IR(0) = 1 # Z = 1 if R0 or R1 is nonzero

testz Rn 1000000n

T1: Z \leftarrow R0(0) OR ... OR R0(7) if IR(0) = 0, \leftarrow R1(0) OR ... OR R1(7) if IR(0) = 1 # Z = 1 if R0 or R1 is nonzero

jump X 10010000 X

J1: MAR \leftarrow PC # Load memory address of jump target

J2: MDR \leftarrow M[MAR] # Fetch jump target address

J3: $PC \leftarrow MDR$ # Jump to target address

jumpz X 10100000 X

JZ1: $MAR \leftarrow PC$ # Load memory address of jump target

JZ2: $MDR \leftarrow M[MAR]$, $PC \leftarrow PC + 1$ # Fetch jump target address and increment PC

JZ3: $PC \leftarrow MDR$ if Z=1 # Jump if Z flag is set

loadsp X 10110000 X

LS1: $MAR \leftarrow PC$ # Load memory address of operand

LS2: $MDR \leftarrow M[MAR]$, $PC \leftarrow PC + 1$ # Fetch operand and increment PC

LS3: $SP \leftarrow MDR$ # Load operand into SP

peek Rn 1100000n

P1: $MAR \leftarrow SP$ # Load address from stack pointer

P2: $MDR \leftarrow M[MAR]$ # Fetch value from stack

P3: $R0 \leftarrow MDR$ if $IR(0) = 0$, $R1 \leftarrow MDR$ if $IR(0) = 1$ # Peek value from stack into R0 if $IR(0) = 0$ else if $IR(0) = 1$ into R1

push Rn 1101000n

PU1: $SP \leftarrow SP - 1$ # Decrement stack pointer

PU2: $MAR \leftarrow SP$ # Load address from stack pointer

PU3: $MDR \leftarrow R0$ if $IR(0) = 0$, $MDR \leftarrow R1$ if $IR(0) = 1$ # Load value from R0 if $IR(0) = 0$ else if $IR(0) = 1$ from R1

PU4: $M[MAR] \leftarrow MDR$ # Push value onto stack

pop Rn 1110000n

PO1: $MAR \leftarrow SP$ # Load address from stack pointer

PO2: $MDR \leftarrow M[MAR]$ # Fetch value from stack

PO3: $R0 \leftarrow MDR$ if $IR(0) = 0$, $R1 \leftarrow MDR$ if $IR(0) = 1$ # Load value into R0 if $IR(0) = 0$ else if $IR(0) = 1$ into R1

+ Microsequencer ROM → ROM Memory Initialization File ↓

```

1  WIDTH=33;
2  DEPTH=256;
3
4  ADDRESS_RADIX=HEX;
5  DATA_RADIX=BIN;
6
7  -- Current Address: UOP(1-24)MAP(8)NEXTADDRESS(7-0)
8  -- 0xADDRESS: 123456789(10)(11)(12)(13)(14)(15)(16)(17)(18)(19)(20)(21)(22)(23)(24)876543210
9
10 CONTENT BEGIN
11 [0..FF]: 00000000000000000000000000000000;
12 00: 0000000000000000000000000000000001;
13 01: 0000001000000000000000000000000010;
14 02: 0100000010000000000000000000000011;
15 03: 00100000000000000000000000100000001;
16 10: 0000001000000000000000000000000010001;
17 11: 0100000010000000000000000000000010010;
18 12: 0000000000100100000000000000000001;
19 20: 00000010000000000000000000000000100001;
20 21: 01000000100000000000000000000000100010;
21 22: 00000110000000000000000000000000100011;
22 23: 00000000100000000000000000000000100100;
23 24: 00000000000100100000000000000000001;
24 30: 00000010000000000000000000000000110001;
25 31: 01000000100000000000000000000000110010;
26 32: 00010110000000000000000000000000110011;
27 33: 00000000110000000000000000000000110100;
28 34: 000100000000000000000000000000000001;
29 40: 0000000001011010000000000000000001;
30 50: 0000000000110111000000000000000001;
31 60: 00000000001101110000000000000000001;
32 70: 0000000000000000010100000000000001;
33 80: 0000000000000000011100000000000001;
34 90: 00000010000000000000000000000010010001;
35 91: 00000000100000000000000000000010010010;
36 92: 0000000000000000000010000000000001;
37 A0: 00000010000000000000000000000010100001;
38 A1: 01000000100000000000000000000010100010;
39 A2: 000000000000000000000000100000000001;
40 B0: 00000010000000000000000000000010110001;
41 B1: 01000000100000000000000000000010110010;
42 B2: 000000000000000000000000100000000001;
43 C0: 000010100000000000000000000011000001;
44 C1: 00000000100000000000000000000011000010;

```

```

00: 0000000000000000000000000000000001;
01: 000000100000000000000000000000000010;
02: 010000001000000000000000000000000011;
03: 001000000000000000000000001000000001;
10: 000000100000000000000000000000000010001;
11: 010000001000000000000000000000000010010;
12: 000000000001001000000000000000000001;
20: 0000001000000000000000000000000000100001;
21: 0100000010000000000000000000000000100010;
22: 0000011000000000000000000000000000100011;
23: 0000000010000000000000000000000000100100;
24: 000000000001001000000000000000000001;
30: 0000001000000000000000000000000000110001;
31: 0100000010000000000000000000000000110010;
32: 0001011000000000000000000000000000110011;
33: 0000000011000000000000000000000000110100;
34: 000100000000000000000000000000000001;
40: 0000000001011010000000000000000001;
50: 0000000000110111000000000000000001;
60: 00000000001101110000000000000000001;
70: 0000000000000000010100000000000001;
80: 0000000000000000011100000000000001;
90: 00000010000000000000000000000010010001;
91: 00000000100000000000000000000010010010;
92: 0000000000000000000010000000000001;
A0: 00000010000000000000000000000010100001;
A1: 01000000100000000000000000000010100010;
A2: 000000000000000000000000100000000001;
B0: 00000010000000000000000000000010110001;
B1: 01000000100000000000000000000010110010;
B2: 000000000000000000000000100000000001;
C0: 000010100000000000000000000011000001;
F0: 100000000000000000000000000000000001;
END;

```

Figure 15: ROM .mif file containing micro-operations for each instruction.

With all components and the ROM initialization file prepared, the final step was synthesizing the microprogrammed CPU on the FPGA. **Figure 16** shows the VHDL implementation of the complete CPU design, which employs structural modeling by instantiating all components with appropriate sizes, pins, control signals, processes, and loops according to the block diagram. A seven-segment display was included to visualize critical values such as register contents, the stack pointer, and the PC.

```

library ieee;
use ieee.std_logic_1164.all;

library lpm;

```



```

use lpm.lpm_components.all;

entity cpu is
    port(
        button, clear: in std_logic;
        Z_FLAG: out std_logic_vector(0 to 0);
        R0SegHi, R0SegLo, R1SegHi, R1SegLo, pcSegHi, pcSegLo, spSegHi, spSegLo:
        out std_logic_vector(0 to 6)
    );
end cpu;

architecture structural of cpu is
    component uSequencer is
        generic(
            uROM_width: integer := 10;
            uROM_file: string := ""
        );
        port(
            opcode: in std_logic_vector(3 downto 0);
            uop: out std_logic_vector(1 to (uROM_width-9));
            debug_map_addr: out std_logic_vector(8 downto 0);
            enable, clear: in std_logic;
            clock: in std_logic
        );
    end component;

    component seven_segment_display is
        port(
            digit: in std_logic_vector(3 downto 0);
            display: out std_logic_vector(0 to 6)

```

```

    );
end component;

-- CLOCK / CONTROL SIGNALS
signal CLOCK, useqEnable, useqClear: std_logic;
signal PC_LOAD, PC_CLEAR, PC_INC, IR_LOAD, WRITE_SEL, MAR_LOAD, MDR_SEL,
MDR_LOAD: std_logic;
signal R0_ENABLE, R0_LOAD, R1_ENABLE, R1_LOAD, ALU_SEL, Z_LOAD, JUMP_SEL,
JUMPZ_SEL: std_logic;
signal SP_ENABLE, SP_LOAD, SP_INC, SP_DEC, M: std_logic;

-- DATA PATH SIGNALS (8-bit registers / ALU)
signal PC_OUT, IR_OUT, MAR_OUT, MEM_OUT, MDR_OUT: std_logic_vector(7 downto 0);
signal MAR_MUX_OUT, MDR_MUX_OUT: std_logic_vector(7 downto 0);
signal R0_OUT, R0_MUX_OUT, R1_OUT, R1_MUX_OUT: std_logic_vector(7 downto 0);
signal ALU_A, ALU_B, ALU_OUT: std_logic_vector(7 downto 0);
signal SP_OUT: std_logic_vector(7 downto 0);

-- MUX SELECT SIGNALS
signal MAR_SEL, MDR_MUX_SEL, R0_SEL, R1_SEL: std_logic_vector(1 downto 0);
signal V_MUX_SEL, V_SEL, Z_SEL: std_logic_vector(0 to 0);

-- 1-BIT MUX
signal V_MUX_0, V_MUX_1: std_logic;
signal V_MUX_OUT, Z_MUX_OUT, Z_OUT: std_logic_vector(0 to 0);

-- MUX DATA ARRAYS
signal MAR_MUX_DATA, MDR_MUX_DATA, R0_MUX_DATA, R1_MUX_DATA: std_logic_2D(3
downto 0, 7 downto 0);
signal V_MUX_DATA, Z_MUX_DATA: std_logic_2D(1 downto 0, 0 to 0);

```

```

-- MICROSEQUENCER / UOP SIGNALS
signal uop: std_logic_vector(1 to 24);
signal m_next_address: std_logic_vector(8 downto 0);

begin
    CLOCK <= not(button);
    delay: lpm_counter
        generic map(lpm_width=>2)
        port map(clock=>CLOCK, cout=>useqEnable);

    useqClear <= clear;
    PC_CLEAR <= uop(1) and useqEnable;
    PC_INC <= uop(2) and useqEnable;
    IR_LOAD <= uop(3);
    WRITE_SEL <= uop(4) and useqEnable;
    MAR_SEL(1) <= uop(5) and useqEnable;
    MAR_SEL(0) <= uop(6) and useqEnable;
    MAR_LOAD <= uop(7) and useqEnable;
    MDR_SEL <= uop(8) and useqEnable;
    MDR_LOAD <= uop(9) and useqEnable;
    R0_SEL(1) <= uop(10) and useqEnable;
    R0_SEL(0) <= uop(11) and useqEnable;
    R0_LOAD <= uop(12) and useqEnable;
    R1_SEL(1) <= uop(13) and useqEnable;
    R1_SEL(0) <= uop(14) and useqEnable;
    R1_LOAD <= uop(15) and useqEnable;
    ALU_SEL <= uop(16) and useqEnable;
    V_SEL(0) <= uop(17) and useqEnable;
    Z_SEL(0) <= uop(18) and useqEnable;

```

```

Z_LOAD <= uop(19) and useqEnable;
JUMP_SEL <= uop(20) and useqEnable;
JUMPZ_SEL <= uop(21) and useqEnable;
SP_LOAD <= uop(22) and useqEnable;
SP_INC <= uop(23) and useqEnable;
SP_DEC <= uop(24) and useqEnable;

PC_LOAD <= (JUMPZ_SEL and Z_OUT(0)) or JUMP_SEL;
R0_ENABLE <= R0_LOAD and not(IR_OUT(0));
R1_ENABLE <= R1_LOAD and IR_OUT(0);
SP_ENABLE <= SP_INC or SP_DEC;
V_MUX_0 <= R0_OUT(0) OR R0_OUT(1) OR R0_OUT(2) OR R0_OUT(3) OR
R0_OUT(4) OR R0_OUT(5) OR R0_OUT(6) OR R0_OUT(7);
V_MUX_1 <= R1_OUT(0) OR R1_OUT(1) OR R1_OUT(2) OR R1_OUT(3) OR
R1_OUT(4) OR R1_OUT(5) OR R1_OUT(6) OR R1_OUT(7);
V_MUX_SEL(0) <= V_SEL(0) and IR_OUT(0);

process (IR_OUT)
begin
    if IR_OUT(0) = '0' then
        ALU_A <= R0_OUT;
        ALU_B <= R1_OUT;
    else
        ALU_A <= R1_OUT;
        ALU_B <= R0_OUT;
    end if;
end process;

PC: lpm_counter
    generic map(lpm_width=>8)

```

```
port map(sload=>PC_LOAD, data=>MDR_OUT, q=>PC_OUT,  
cnt_en=>PC_INC, sclr=>PC_CLEAR, clock=>CLOCK);
```

IR: lpm_ff

```
generic map(lpm_width=>8)  
port map(enable=>IR_LOAD, data=>MDR_OUT, q=>IR_OUT,  
clock=>CLOCK);
```

uSeq: uSequencer

```
generic map(uROM_width=>33, uROM_file=>"rom.mif")  
port map(opcode=>IR_OUT(7 downto 4), uop=>uop,  
debug_map_addr=>m_next_address, enable=>useqEnable, clear=>useqClear,  
clock=>CLOCK);
```

MAR_MUX_LOOP: for i in 0 to 7 generate

```
MAR_MUX_DATA(0, i) <= PC_OUT(i);  
MAR_MUX_DATA(1, i) <= MDR_OUT(i);  
MAR_MUX_DATA(2, i) <= SP_OUT(i);  
MAR_MUX_DATA(3, i) <= '0';
```

end generate;

MAR_MUX: lpm_mux

```
generic map(lpm_width=>8, lpm_size=>4, lpm_widths=>2)  
port map(data=>MAR_MUX_DATA, result=>MAR_MUX_OUT,  
sel=>MAR_SEL);
```

MAR: lpm_ff

```
generic map(lpm_width=>8)  
port map(enable=>MAR_LOAD, data=>MAR_MUX_OUT, q=>MAR_OUT,  
clock=>CLOCK);
```

```
RAM: lpm_ram_dq
    generic map(lpm_widthad=>8, lpm_width=>8, lpm_file=>"ram.mif")
    port map(address=>MAR_OUT, data=>MDR_OUT, q=>MEM_OUT,
inclock=>CLOCK, outclock=>CLOCK, we=>WRITE_SEL);
```

```
MDR_MUX_LOOP: for i in 0 to 7 generate
    MDR_MUX_DATA(0, i) <= MEM_OUT(i);
    MDR_MUX_DATA(1, i) <= R0_OUT(i);
    MDR_MUX_DATA(2, i) <= MEM_OUT(i);
    MDR_MUX_DATA(3, i) <= R1_OUT(i);
end generate;
```

```
MDR_MUX: lpm_mux
    generic map(lpm_width=>8, lpm_size=>4, lpm_widths=>2)
    port map(data=>MDR_MUX_DATA, result=>MDR_MUX_OUT,
sel=>(IR_OUT(0) & MDR_SEL));
```

```
MDR: lpm_ff
    generic map(lpm_width=>8)
    port map(enable=>MDR_LOAD, data=>MDR_MUX_OUT, q=>MDR_OUT,
clock=>CLOCK);
```

```
ALU: lpm_add_sub
    generic map (lpm_width=>8)
    port map (dataa=>ALU_A, datab=>ALU_B, result=>ALU_OUT,
add_sub=>ALU_SEL);
```

```
R0_MUX_LOOP: for i in 0 to 7 generate
    R0_MUX_DATA(0, i) <= MDR_OUT(i);
```

```

        R0_MUX_DATA(1, i) <= ALU_OUT(i);
        R0_MUX_DATA(2, i) <= R1_OUT(i);
        R0_MUX_DATA(3, i) <= '0';
    end generate;

R0_MUX: lpm_mux
    generic map(lpm_width=>8, lpm_size=>4, lpm_widths=>2)
    port map(data=>R0_MUX_DATA, result=>R0_MUX_OUT, sel=>R0_SEL);

REG0: lpm_ff
    generic map(lpm_width=>8)
    port map(enable=>R0_ENABLE, data=>R0_MUX_OUT, q=>R0_OUT,
clock=>CLOCK);

R1_MUX_LOOP: for i in 0 to 7 generate
    R1_MUX_DATA(0, i) <= MDR_OUT(i);
    R1_MUX_DATA(1, i) <= ALU_OUT(i);
    R1_MUX_DATA(2, i) <= R0_OUT(i);
    R1_MUX_DATA(3, i) <= '0';
end generate;

R1_MUX: lpm_mux
    generic map(lpm_width=> 8, lpm_size=> 4, lpm_widths=> 2)
    port map(data=>R1_MUX_DATA, result=>R1_MUX_OUT, sel=>R1_SEL);

REG1: lpm_ff
    generic map(lpm_width=>8)
    port map(enable=>R1_ENABLE, data=>R1_MUX_OUT, q=>R1_OUT,
clock=>CLOCK);

```

```

STACK_POINTER: lpm_counter
    generic map(lpm_width=>8)
    port map(sload=>SP_LOAD, data=>MDR_OUT, q=>SP_OUT,
cnt_en=>SP_ENABLE, updown=>SP_INC, clock=>CLOCK);

V_MUX_DATA(0, 0) <= V_MUX_0;
V_MUX_DATA(1, 0) <= V_MUX_1;

V_MUX: lpm_mux
    generic map(lpm_width=>1, lpm_size=>2, lpm_widths=>1)
    port map(data=>V_MUX_DATA, result=>V_MUX_OUT, sel=>V_MUX_SEL);

Z_MUX_DATA(0, 0) <= not V_MUX_OUT(0);
Z_MUX_DATA(1, 0) <= V_MUX_OUT(0);

Z_MUX: lpm_mux
    generic map(lpm_width=>1, lpm_size=>2, lpm_widths=>1)
    port map(data=>Z_MUX_DATA, result=>Z_MUX_OUT, sel=>Z_SEL);

REG_Z: lpm_ff
    generic map(lpm_width=>1)
    port map(enable=>Z_LOAD, data=>Z_MUX_OUT, q=>Z_OUT,
clock=>CLOCK);

Z_FLAG <= Z_OUT;

R0Hi: seven_segment_display port map(digit=>R0_OUT(7 downto 4),
display=>R0SegHi);
R0Lo: seven_segment_display port map(digit=>R0_OUT(3 downto 0),
display=>R0SegLo);

```



```

        R1Hi: seven_segment_display port map(digit=>R1_OUT(7 downto 4),
display=>R1SegHi);
        R1Lo: seven_segment_display port map(digit=>R1_OUT(3 downto 0),
display=>R1SegLo);
        pcHi: seven_segment_display port map(digit=>PC_OUT(7 downto 4),
display=>pcSegHi);
        pcLo: seven_segment_display port map(digit=>PC_OUT(3 downto 0),
display=>pcSegLo);
        spHi: seven_segment_display port map(digit=>SP_OUT(7 downto 4),
display=>spSegHi);
        spLo: seven_segment_display port map(digit=>SP_OUT(3 downto 0),
display=>spSegLo);

end structural;

```

Figure 16: VHDL implementation of the full microprogrammed CPU on the FPGA, including seven-segment displays.

✚ FPGA Pin Layout

Figure 17: Signal Number and its corresponding Pin Number on the *Altera Cyclone® IV EP4CE115F29C7* FPGA.

	Node Name	Direction	Location
in	button	Input	PIN_M21
in	clear	Input	PIN_Y23
out	R0SeqHi[0]	Output	PIN_M24
out	R0SeqHi[1]	Output	PIN_Y22
out	R0SeqHi[2]	Output	PIN_W21
out	R0SeqHi[3]	Output	PIN_W22
out	R0SeqHi[4]	Output	PIN_W25
out	R0SeqHi[5]	Output	PIN_U23
out	R0SeqHi[6]	Output	PIN_U24
out	R0SeqLo[0]	Output	PIN_G18
out	R0SeqLo[1]	Output	PIN_F22
out	R0SeqLo[2]	Output	PIN_E17
out	R0SeqLo[3]	Output	PIN_L26
out	R0SeqLo[4]	Output	PIN_L25
out	R0SeqLo[5]	Output	PIN_J22
out	R0SeqLo[6]	Output	PIN_H22
out	R1SeqHi[0]	Output	PIN_V21
out	R1SeqHi[1]	Output	PIN_U21
out	R1SeqHi[2]	Output	PIN_AB20
out	R1SeqHi[3]	Output	PIN_AA21
out	R1SeqHi[4]	Output	PIN_AD24
out	R1SeqHi[5]	Output	PIN_AF23
out	R1SeqHi[6]	Output	PIN_Y19
out	R1SeqLo[0]	Output	PIN_AA25
out	R1SeqLo[1]	Output	PIN_AA26
out	R1SeqLo[2]	Output	PIN_Y25
out	R1SeqLo[3]	Output	PIN_W26
out	R1SeqLo[4]	Output	PIN_Y26
out	R1SeqLo[5]	Output	PIN_W27
out	R1SeqLo[6]	Output	PIN_W28
out	Z_FLAG[0]	Output	PIN_H15
out	pcSeqHi[0]	Output	PIN_AD18
out	pcSeqHi[1]	Output	PIN_AC18
out	pcSeqHi[2]	Output	PIN_AB18
out	pcSeqHi[3]	Output	PIN_AH19
out	pcSeqHi[4]	Output	PIN_AG19
out	pcSeqHi[5]	Output	PIN_AF18
out	pcSeqHi[6]	Output	PIN_AH18
out	pcSeqLo[0]	Output	PIN_AB19
out	pcSeqLo[1]	Output	PIN_AA19
out	pcSeqLo[2]	Output	PIN_AG21
out	pcSeqLo[3]	Output	PIN_AH21
out	pcSeqLo[4]	Output	PIN_AE19
out	pcSeqLo[5]	Output	PIN_AF19
out	pcSeqLo[6]	Output	PIN_AE18
out	spSeqHi[0]	Output	PIN_AD17
out	spSeqHi[1]	Output	PIN_AE17
out	spSeqHi[2]	Output	PIN_AG17
out	spSeqHi[3]	Output	PIN_AH17
out	spSeqHi[4]	Output	PIN_AF17
out	spSeqHi[5]	Output	PIN_AG18
out	spSeqHi[6]	Output	PIN_AA14
out	spSeqLo[0]	Output	PIN_AA17
out	spSeqLo[1]	Output	PIN_AB16
out	spSeqLo[2]	Output	PIN_AA16
out	spSeqLo[3]	Output	PIN_AB17
out	spSeqLo[4]	Output	PIN_AB15
out	spSeqLo[5]	Output	PIN_AA15
out	spSeqLo[6]	Output	PIN_AC17

Figure 18: Final Pin Assignments for the Microprogrammed CPU Design Implementation on the FPGA Board.

RESULTS AND DISCUSSION

Before implementing the full CPU design in VHDL, we first verified the functionality of the microsequencer independently. Using the tests described in the Theory and Methods section, we hardwired opcodes and initialized the ROM with .mif files to exercise specific sequences of micro-operations. During these tests, the seven-segment display was used to visualize the values of key registers, the program counter (PC), and outputs, providing a straightforward way to confirm that control signals were being correctly generated and that the microsequencer executed microinstructions in the expected order. These tests confirmed that the microsequencer correctly handled address sequencing, mapping signals, and control signal activation, forming a reliable foundation for the CPU implementation.

Following the successful verification of the microsequencer, we proceeded to test the RAM subsystem. By initializing RAM with .mif files and running simple load and store operations in conjunction with the microsequencer, we were able to validate proper data transfer between registers and memory, as well as the correct operation of address and data buses. The seven-segment display continued to serve as a key debugging tool, allowing real-time monitoring of register values, memory contents, and intermediate outputs.

Once both the microsequencer and RAM were verified, we integrated these components into the full CPU VHDL design. To validate the complete system, we utilized the collection of RAM files provided by our professor, which contained sequences covering all 16 CPU instructions (**Figure 19**). Running the CPU design with each of these files allowed us to verify that every instruction executed correctly without any modifications to the VHDL code. This demonstrates that our design is truly general-purpose: the CPU executes the full instruction set as intended without being tailored to specific instructions, reflecting the behavior expected of a functional, programmable processor.

We presented our design in person to our professor, demonstrating the CPU running each RAM file and verifying proper functionality across all instructions. The professor provided written approval as confirmation of successful verification. The ability to execute all

instructions with a single, unmodified CPU design highlights the correctness and robustness of our implementation, as well as the effectiveness of our testing methodology using the microsequencer, RAM, and seven-segment display for debugging.

 ram_files

Figure 19: Folder containing RAM files provided by the professor, used to test the CPU design with all 16 instructions and verify functionality across the full instruction set.

CONCLUSIONS

Throughout this project, we leveraged the seven-segment display as a key debugging tool, frequently changing which values were displayed to monitor the inputs and outputs of specific components as we progressed through testing the RAM files. This iterative approach allowed us to identify and correct potential issues at the microsequencer, RAM, and CPU levels, ensuring that each component functioned as intended.

Ultimately, our final VHDL implementation successfully executed every instruction in the CPU's instruction set, regardless of how the instructions were programmed in the RAM. This demonstrated that our design is fully general-purpose and capable of handling a complete range of operations without modification, reflecting the principles of a functional and programmable CPU.

This project provided an invaluable hands-on experience in computer architecture and digital design. By designing, testing, and debugging a microprogrammed CPU on an FPGA, we gained practical insight into the interaction between control units, memory, and the execution of instructions. Such experience is crucial for computer engineering students, as it bridges theoretical knowledge with practical skills needed to understand and implement the core elements of modern processors.


REFERENCES

1. ECE495 Slides by Edwin Hou


APPENDIX

- Block Diagrams


CPU Block Diagram

 


Microsequencer Block Diagram

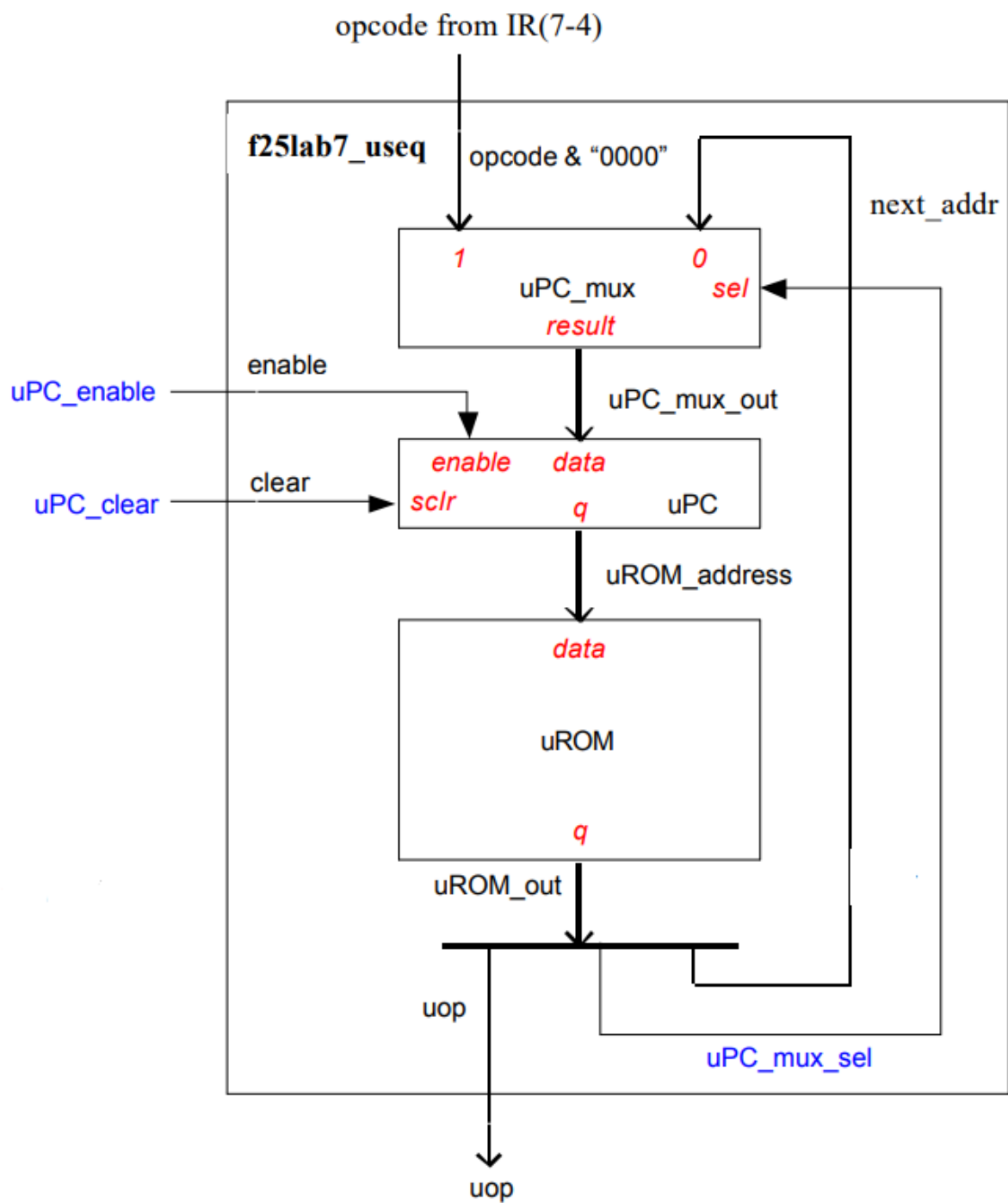

RAM Block Diagram

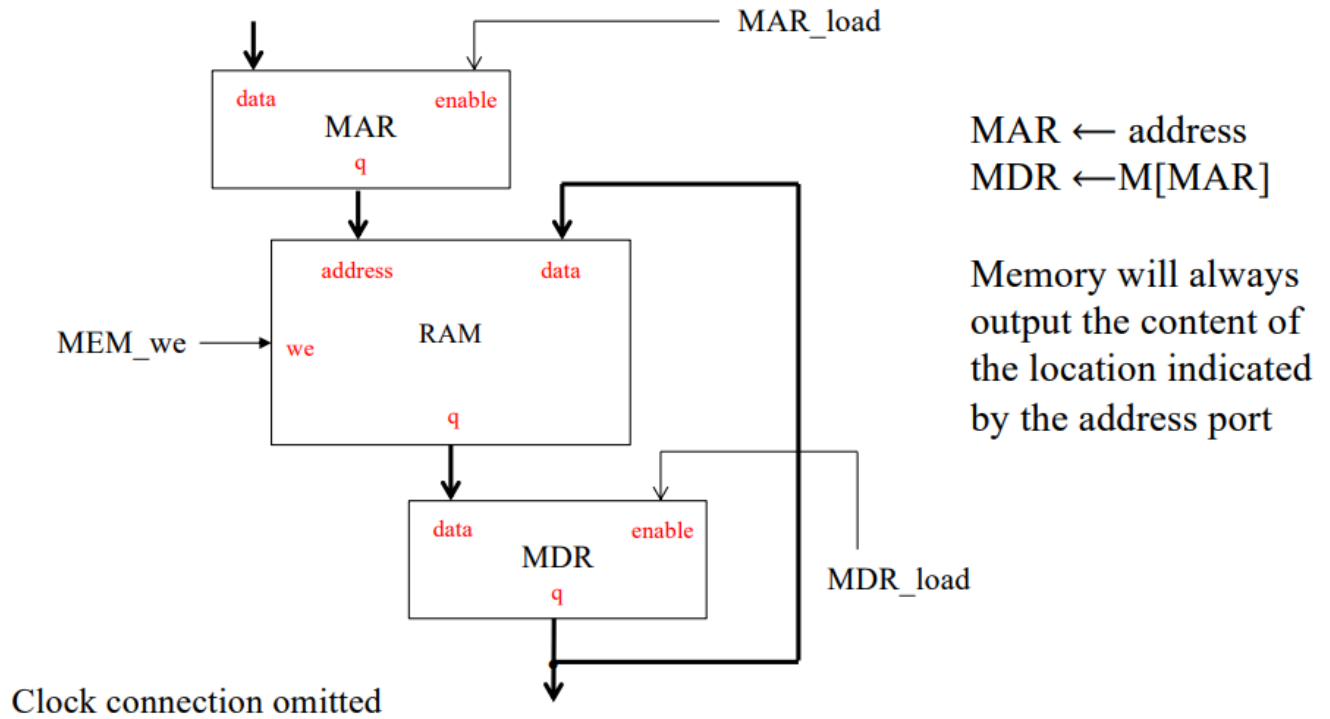

Microprogrammed CPU Design Block Diagram

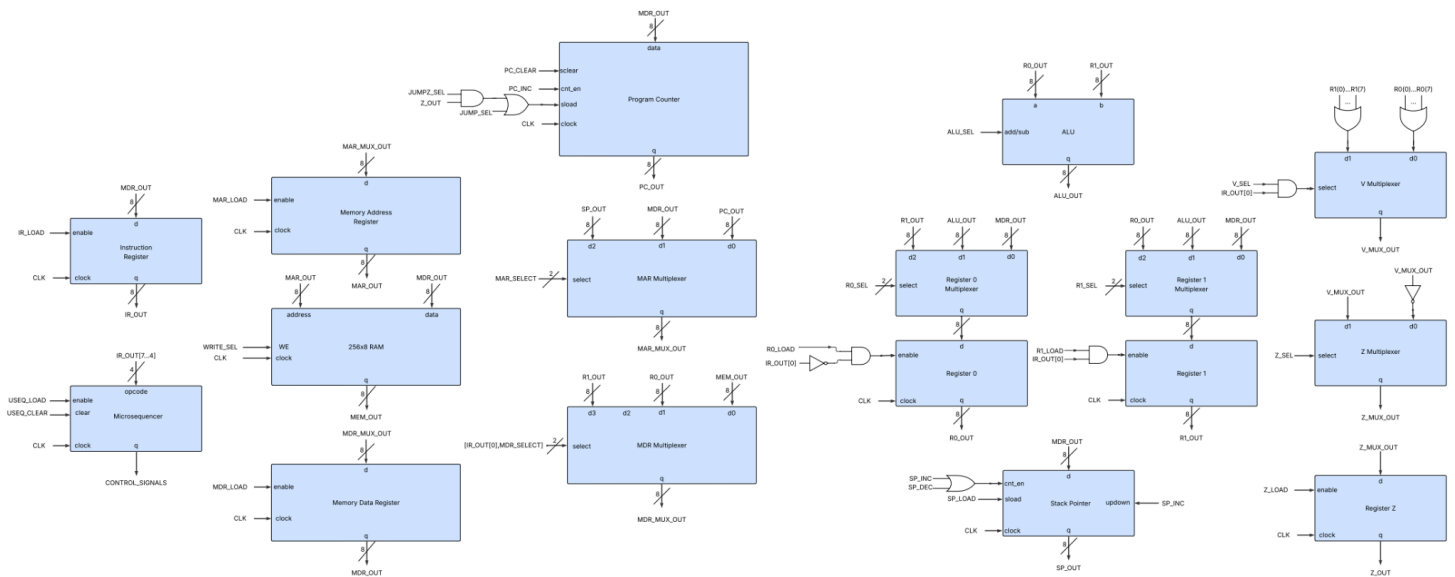

- Source Code

Microsequencer Component

```
library ieee;
use ieee.std_logic_1164.all;
library lpm;
use lpm.lpm_components.all;

entity uSequencer is
  generic(
    uROM_width: integer := 10;
    uROM_file: string := ""
  );
  port(
    opcode: in std_logic_vector(3 downto 0);
    uop: out std_logic_vector(1 to (uROM_width-9));
    debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging
    enable, clear: in std_logic;
    clock: in std_logic
  );
end uSequencer;

architecture structural of uSequencer is
  signal uROM_address: std_logic_vector (7 downto 0);
  signal uROM_out: std_logic_vector (uROM_width-1 downto 0);
  signal uPC_mux_data: std_logic_2D(1 downto 0, 7 downto 0);
  signal uPC_mux_sel: std_logic_vector(0 to 0);
  signal uPC_mux_out: std_logic_vector(7 downto 0);
  signal temp: std_logic_vector(7 downto 0);
```



```

begin
    temp <= opcode & "0000";

    for_label: for i in 0 to 7 generate
        uPC_mux_data(0, i) <= uROM_out(i);
        uPC_mux_data(1, i) <= temp(i);
    end generate;

    uPC_mux_sel(0) <= uROM_out(8);

    uPC_mux: lpm_mux
        generic map (lpm_width=>8, lpm_size=>2, lpm_widths=>1)
        port map (result=>uPC_mux_out, data=>uPC_mux_data, sel=>uPC_mux_sel);
    uPC: lpm_ff
        generic map (lpm_width=>8)
        port map (clock=>clock, data=>uPC_mux_out, q=>uROM_address, sclr=>clear,
enable=>enable);
    uROM: lpm_rom
        generic map (lpm_widthad=>8, lpm_width=>uROM_width, lpm_file=>uROM_file)
        port map (address=>uROM_address, q=>uROM_out, inclock=>clock,
outclock=>clock);

    uop <= uROM_out(uROM_width-1 downto 9);
    debug_map_addr <= uROM_out(8 downto 0);
end structural;

```

Test Microsequencer without PC Register

```

library ieee;
use ieee.std_logic_1164.all;

```

```

library lpm;
use lpm.lpm_components.all;

entity test_uSequencer is
    port(
        button, clear: in std_logic;
        useqEnOut: out std_logic;
        ctrlSignals: out std_logic_vector(0 to 7);
        M_disp, disp1, disp0: out std_logic_vector(0 to 6)
    );
end test_uSequencer;

architecture structural of test_uSequencer is
    component uSequencer is
        generic(
            uROM_width: integer := 10;
            uROM_file: string := ""
        );
        port(
            opcode: in std_logic_vector(3 downto 0);
            uop: out std_logic_vector(1 to (uROM_width-9));
            debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging
            enable, clear: in std_logic;
            clock: in std_logic
        );
    end component;

    component seven_segment_display is
        port(
            digit: in std_logic_vector(3 downto 0);

```

```

        display: out std_logic_vector(0 to 6)
    );
end component;

signal useqEnable, useqClear, clk: std_logic;
signal uop: std_logic_vector(0 to 7);
signal address_out: std_logic_vector(8 downto 0);
signal M, addr_hex1, addr_hex0: std_logic_vector(3 downto 0);
begin
    clk <= not(button);
    delay: lpm_counter generic map(lpm_width=>2) port map(clock=>clk,
cout=>useqEnable);

    useqClear <= clear;
    useqEnOut <= useqEnable;

    labelG: for i in 0 to 7 generate
        ctrlSignals(i) <= uop(i) and useqEnable;
    end generate;

    uSeq: uSequencer
        generic map(uROM_width=>17, uROM_file=>"test_uSequencer_file.mif")
        port map(opcode=>"0011", uop=>uop, debug_map_addr=>address_out,
enable=>useqEnable, clear=>useqClear, clock=>clk);

    M <= "000" & address_out(8);
    addr_hex1 <= address_out(7 downto 4);
    addr_hex0 <= address_out(3 downto 0);
    display1: seven_segment_display port map(digit=>M, display=>M_disp);

```

```

display2: seven_segment_display port map(digit=>addr_hex1, display=>disp1);
display3: seven_segment_display port map(digit=>addr_hex0, display=>disp0);
end structural;

```

Test Microsequencer with PC Register

```

library ieee;
use ieee.std_logic_1164.all;
library lpm;
use lpm.lpm_components.all;

entity test_uSequencer_PC is
    port(
        button, clear: in std_logic;
        useqEnOut: out std_logic;
        ctrlSignals: out std_logic_vector(0 to 7);
        pc_Seg1, pc_Seg0, M_disp, disp1, disp0: out std_logic_vector(0 to 6)
    );
end test_uSequencer_PC;

architecture structural of test_uSequencer_PC is
    component uSequencer is
        generic(
            uROM_width: integer := 10;
            uROM_file: string := ""
        );
        port(
            opcode: in std_logic_vector(3 downto 0);
            uop: out std_logic_vector(1 to (uROM_width-9));
            debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging

```

```

    enable, clear: in std_logic;
    clock: in std_logic
);
end component;

component seven_segment_display is
    port(
        digit: in std_logic_vector(3 downto 0);
        display: out std_logic_vector(0 to 6)
    );
end component;

signal useqEnable, useqClear, clk: std_logic;
signal pcInc, pcLoad, pcClear: std_logic;
signal pcOut: std_logic_vector(7 downto 0);
signal uop: std_logic_vector(0 to 7);
signal address_out: std_logic_vector(8 downto 0);
signal M, addr_hex1, addr_hex0, pc_hex1, pc_hex0: std_logic_vector(3 downto 0);
begin
    clk <= not(button);
    delay: lpm_counter
        generic map(lpm_width=>2)
        port map(clock=>clk, cout=>useqEnable);

    useqClear <= clear;
    useqEnOut <= useqEnable;

    labelG: for i in 0 to 7 generate
        ctrlSignals(i) <= uop(i) and useqEnable;
    end generate;

```

```

pcInc <= uop(0) and useqEnable;
pcLoad <= uop(1) and useqEnable;
pcClear <= uop(2) and useqEnable;

uSeq: uSequencer
    generic map(uROM_width=>17,
uROM_file=>"test_uSequencer_PC_file.mif")
        port map(opcode=>"0011", uop=>uop, debug_map_addr=>address_out,
enable=>useqEnable, clear=>useqClear, clock=>clk);

pc: lpm_counter
    generic map(lpm_width=>8)
        port map(sload=>pcLoad, data=> "10101010", q=>pcOut, cnt_en=>pcInc,
sclr=>pcClear, clock=>clk);

M <= "000" & address_out(8);
addr_hex1 <= address_out(7 downto 4);
addr_hex0 <= address_out(3 downto 0);
pc_hex1 <= pcOut(7 downto 4);
pc_hex0 <= pcOut(3 downto 0);
display1: seven_segment_display port map(digit=>M, display=>M_disp);
display2: seven_segment_display port map(digit=>addr_hex1, display=>disp1);
display3: seven_segment_display port map(digit=>addr_hex0, display=>disp0);
display4: seven_segment_display port map(digit=>pc_hex1, display=>pc_Seg1);
display5: seven_segment_display port map(digit=>pc_hex0, display=>pc_Seg0);

end structural;

```

Read and Write to/from RAM using MicroSequencer

```
library ieee;
use ieee.std_logic_1164.all;

library lpm;
use lpm.lpm_components.all;

entity test_ram is
    port(
        button, clear: in std_logic;
        useqEnOut: out std_logic;
        marData: in std_logic_vector(7 downto 0); -- connected to switches, input
to MAR
        marSegHi, marSegLo, mdrSegHi, mdrSegLo, nextAddrHi, nextAddrLo: out
std_logic_vector(0 to 6);
        ctrlSignals: out std_logic_vector(0 to 7)
    );
end test_ram;

architecture structural of test_ram is
    component uSequencer is
        generic(
            uROM_width: integer := 10;
            uROM_file: string := ""
        );
        port(
            opcode: in std_logic_vector(3 downto 0);
            uop: out std_logic_vector(1 to (uROM_width-9));
            debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging
            enable, clear: in std_logic;
            clock: in std_logic
```

```

);
end component;

component seven_segment_display is
    port(
        digit: in std_logic_vector(3 downto 0);
        display: out std_logic_vector(0 to 6)
    );
end component;

signal clk, useqEnable, useqClear, marLoad, mdrLoad, memWE: std_logic;
signal uop: std_logic_vector(0 to 7);
signal marADig, marBDig, mdrADig, mdrBDig, nextAADig, nextABDig: std_logic_vector(3
downto 0);
signal marOut, memOut, mdrOut: std_logic_vector(7 downto 0);
signal address_out: std_logic_vector(8 downto 0);
begin
    clk <= not(button);
    useqClear <= clear;
    useqEnOut <= useqEnable;
    marLoad <= uop(0) and useqEnable;
    mdrLoad <= uop(1) and useqEnable;
    memWE <= uop(2) and useqEnable;

    marADig <= marOut(7 downto 4);
    marBDig <= marOut(3 downto 0);
    mdrADig <= mdrOut(7 downto 4);
    mdrBDig <= mdrOut(3 downto 0);
    nextAADig <= address_out(7 downto 4);
    nextABDig <= address_out(3 downto 0);

```



```

labelG: for i in 0 to 7 generate
    ctrlSignals(i) <= uop(i) and useqEnable;
end generate;

delay: lpm_counter generic map(lpm_width=>2) port map(clock=>clk,
cout=>useqEnable);

microSequencer: uSequencer
    generic map(uROM_width=>17, uROM_file=>"test_rom_file.mif")
    port map(opcode=>"0000", uop=>uop, debug_map_addr=>address_out,
enable=>useqEnable, clear=>useqClear, clock=>clk);

marReg: lpm_ff
    generic map(lpm_width=>8)
    port map(data=>marData, q=>marOut, clock=>clk, enable=>marLoad);

mdrReg: lpm_ff
    generic map(lpm_width=>8)
    port map(data=>memOut, q=>mdrOut, clock=>clk, enable=>mdrLoad);

ram: lpm_ram_dq
    generic map(lpm_widthad=>8, lpm_width=>8,
lpm_file=>"test_ram_file.mif")
    port map(data=>mdrOut, address=>marOut, q=>memOut, inclock=>clk,
outclock=>clk, we=>memWE);

marA: seven_segment_display port map(digit=>marADig, display=>marSegHi);
marB: seven_segment_display port map(digit=>marBDig, display=>marSegLo);
mdrA: seven_segment_display port map(digit=>mdrADig, display=>mdrSegHi);
mdrB: seven_segment_display port map(digit=>mdrBDig, display=>mdrSegLo);
nextAddressA: seven_segment_display port map(digit=>nextAADig,
display=>nextAddrHi);
nextAddressB: seven_segment_display port map(digit=>nextABDig,
display=>nextAddrLo);

```

```
end structural;
```

Seven Segment Display Component

```
library IEEE;
use IEEE.std_logic_1164.all;

entity seven_segment_display is
    port(
        digit: in std_logic_vector(3 downto 0);
        display: out std_logic_vector(0 to 6)
    );
end seven_segment_display;

architecture behavior of seven_segment_display is
begin
    with digit select
        display <= "0000001" when "0000",
                   "1001111" when "0001",
                   "0010010" when "0010",
                   "0000110" when "0011",
                   "1001100" when "0100",
                   "0100100" when "0101",
                   "0100000" when "0110",
                   "0001111" when "0111",
                   "0000000" when "1000",
                   "0000100" when "1001",
                   "0001000" when "1010",
                   "1100000" when "1011",
                   "0110001" when "1100",
```

```

        "1000010" when "1101",
        "0110000" when "1110",
        "0111000" when "1111",
        "1111111" when others;
end behavior;

```

Microsequencer-based CPU

```

library ieee;
use ieee.std_logic_1164.all;
library lpm;
use lpm.lpm_components.all;

entity cpu is
    port(
        button, clear: in std_logic;
        Z_FLAG: out std_logic_vector(0 to 0);
        R0SegHi, R0SegLo, R1SegHi, R1SegLo, pcSegHi, pcSegLo, spSegHi, spSegLo:
        out std_logic_vector(0 to 6)
    );
end cpu;

architecture structural of cpu is
    component uSequencer is
        generic(
            uROM_width: integer := 10;
            uROM_file: string := ""
        );
        port(
            opcode: in std_logic_vector(3 downto 0);

```

```

        uop: out std_logic_vector(1 to (uROM_width-9));
        debug_map_addr: out std_logic_vector(8 downto 0);
        enable, clear: in std_logic;
        clock: in std_logic
    );
end component;

component seven_segment_display is
    port(
        digit: in std_logic_vector(3 downto 0);
        display: out std_logic_vector(0 to 6)
    );
end component;

-- CLOCK / CONTROL SIGNALS
signal CLOCK, useqEnable, useqClear: std_logic;
signal PC_LOAD, PC_CLEAR, PC_INC, IR_LOAD, WRITE_SEL, MAR_LOAD, MDR_SEL,
MDR_LOAD: std_logic;
signal R0_ENABLE, R0_LOAD, R1_ENABLE, R1_LOAD, ALU_SEL, Z_LOAD, JUMP_SEL,
JUMPZ_SEL: std_logic;
signal SP_ENABLE, SP_LOAD, SP_INC, SP_DEC, M: std_logic;

-- DATA PATH SIGNALS (8-bit registers / ALU)
signal PC_OUT, IR_OUT, MAR_OUT, MEM_OUT, MDR_OUT: std_logic_vector(7 downto 0);
signal MAR_MUX_OUT, MDR_MUX_OUT: std_logic_vector(7 downto 0);
signal R0_OUT, R0_MUX_OUT, R1_OUT, R1_MUX_OUT: std_logic_vector(7 downto 0);
signal ALU_A, ALU_B, ALU_OUT: std_logic_vector(7 downto 0);
signal SP_OUT: std_logic_vector(7 downto 0);

-- MUX SELECT SIGNALS

```

```

signal MAR_SEL, MDR_MUX_SEL, R0_SEL, R1_SEL: std_logic_vector(1 downto 0);
signal V_MUX_SEL, V_SEL, Z_SEL: std_logic_vector(0 to 0);

-- 1-BIT MUX
signal V_MUX_0, V_MUX_1: std_logic;
signal V_MUX_OUT, Z_MUX_OUT, Z_OUT: std_logic_vector(0 to 0);

-- MUX DATA ARRAYS
signal MAR_MUX_DATA, MDR_MUX_DATA, R0_MUX_DATA, R1_MUX_DATA: std_logic_2D(3
downto 0, 7 downto 0);
signal V_MUX_DATA, Z_MUX_DATA: std_logic_2D(1 downto 0, 0 to 0);

-- MICROSEQUENCER / UOP SIGNALS
signal uop: std_logic_vector(1 to 24);
signal m_next_address: std_logic_vector(8 downto 0);

begin
    CLOCK <= not(button);
    delay: lpm_counter
        generic map(lpm_width=>2)
        port map(clock=>CLOCK, cout=>useqEnable);

    useqClear <= clear;
    PC_CLEAR <= uop(1) and useqEnable;
    PC_INC <= uop(2) and useqEnable;
    IR_LOAD <= uop(3);
    WRITE_SEL <= uop(4) and useqEnable;
    MAR_SEL(1) <= uop(5) and useqEnable;
    MAR_SEL(0) <= uop(6) and useqEnable;
    MAR_LOAD <= uop(7) and useqEnable;

```

```
MDR_SEL <= uop(8) and useqEnable;
MDR_LOAD <= uop(9) and useqEnable;
R0_SEL(1) <= uop(10) and useqEnable;
R0_SEL(0) <= uop(11) and useqEnable;
R0_LOAD <= uop(12) and useqEnable;
R1_SEL(1) <= uop(13) and useqEnable;
R1_SEL(0) <= uop(14) and useqEnable;
R1_LOAD <= uop(15) and useqEnable;
ALU_SEL <= uop(16) and useqEnable;
V_SEL(0) <= uop(17) and useqEnable;
Z_SEL(0) <= uop(18) and useqEnable;
Z_LOAD <= uop(19) and useqEnable;
JUMP_SEL <= uop(20) and useqEnable;
JUMPZ_SEL <= uop(21) and useqEnable;
SP_LOAD <= uop(22) and useqEnable;
SP_INC <= uop(23) and useqEnable;
SP_DEC <= uop(24) and useqEnable;
```

```
PC_LOAD <= (JUMPZ_SEL and Z_OUT(0)) or JUMP_SEL;
R0_ENABLE <= R0_LOAD and not(IR_OUT(0));
R1_ENABLE <= R1_LOAD and IR_OUT(0);
SP_ENABLE <= SP_INC or SP_DEC;
V_MUX_0 <= R0_OUT(0) OR R0_OUT(1) OR R0_OUT(2) OR R0_OUT(3) OR
R0_OUT(4) OR R0_OUT(5) OR R0_OUT(6) OR R0_OUT(7);
V_MUX_1 <= R1_OUT(0) OR R1_OUT(1) OR R1_OUT(2) OR R1_OUT(3) OR
R1_OUT(4) OR R1_OUT(5) OR R1_OUT(6) OR R1_OUT(7);
V_MUX_SEL(0) <= V_SEL(0) and IR_OUT(0);
```

```
process (IR_OUT)
```

```
begin
```

```

    if IR_OUT(0) = '0' then
        ALU_A <= R0_OUT;
        ALU_B <= R1_OUT;
    else
        ALU_A <= R1_OUT;
        ALU_B <= R0_OUT;
    end if;
end process;

```

```

PC: lpm_counter
    generic map(lpm_width=>8)
    port map(sload=>PC_LOAD, data=>MDR_OUT, q=>PC_OUT,
cnt_en=>PC_INC, sclr=>PC_CLEAR, clock=>CLOCK);

```

```

IR: lpm_ff
    generic map(lpm_width=>8)
    port map(enable=>IR_LOAD, data=>MDR_OUT, q=>IR_OUT,
clock=>CLOCK);

```

```

uSeq: uSequencer
    generic map(uROM_width=>33, uROM_file=>"rom.mif")
    port map(opcode=>IR_OUT(7 downto 4), uop=>uop,
debug_map_addr=>m_next_address, enable=>useqEnable, clear=>useqClear,
clock=>CLOCK);

```

```

MAR_MUX_LOOP: for i in 0 to 7 generate
    MAR_MUX_DATA(0, i) <= PC_OUT(i);
    MAR_MUX_DATA(1, i) <= MDR_OUT(i);
    MAR_MUX_DATA(2, i) <= SP_OUT(i);
    MAR_MUX_DATA(3, i) <= '0';
end generate

```

```

end generate;

MAR_MUX: lpm_mux
    generic map(lpm_width=>8, lpm_size=>4, lpm_widths=>2)
    port map(data=>MAR_MUX_DATA, result=>MAR_MUX_OUT,
sel=>MAR_SEL);

MAR: lpm_ff
    generic map(lpm_width=>8)
    port map(enable=>MAR_LOAD, data=>MAR_MUX_OUT, q=>MAR_OUT,
clock=>CLOCK);

RAM: lpm_ram_dq
    generic map(lpm_widthad=>8, lpm_width=>8, lpm_file=>"ram.mif")
    port map(address=>MAR_OUT, data=>MDR_OUT, q=>MEM_OUT,
inclock=>CLOCK, outclock=>CLOCK, we=>WRITE_SEL);

MDR_MUX_LOOP: for i in 0 to 7 generate
    MDR_MUX_DATA(0, i) <= MEM_OUT(i);
    MDR_MUX_DATA(1, i) <= R0_OUT(i);
    MDR_MUX_DATA(2, i) <= MEM_OUT(i);
    MDR_MUX_DATA(3, i) <= R1_OUT(i);
end generate;

MDR_MUX: lpm_mux
    generic map(lpm_width=>8, lpm_size=>4, lpm_widths=>2)
    port map(data=>MDR_MUX_DATA, result=>MDR_MUX_OUT,
sel=>(IR_OUT(0) & MDR_SEL));

MDR: lpm_ff

```



```
generic map(lpm_width=>8)
port map(enable=>MDR_LOAD, data=>MDR_MUX_OUT, q=>MDR_OUT,
clock=>CLOCK);
```

```
ALU: lpm_add_sub
generic map (lpm_width=>8)
port map (dataa=>ALU_A, datab=>ALU_B, result=>ALU_OUT,
add_sub=>ALU_SEL);
```

```
R0_MUX_LOOP: for i in 0 to 7 generate
    R0_MUX_DATA(0, i) <= MDR_OUT(i);
    R0_MUX_DATA(1, i) <= ALU_OUT(i);
    R0_MUX_DATA(2, i) <= R1_OUT(i);
    R0_MUX_DATA(3, i) <= '0';
end generate;
```

```
R0_MUX: lpm_mux
generic map(lpm_width=>8, lpm_size=>4, lpm_widths=>2)
port map(data=>R0_MUX_DATA, result=>R0_MUX_OUT, sel=>R0_SEL);
```

```
REG0: lpm_ff
generic map(lpm_width=>8)
port map(enable=>R0_ENABLE, data=>R0_MUX_OUT, q=>R0_OUT,
clock=>CLOCK);
```

```
R1_MUX_LOOP: for i in 0 to 7 generate
    R1_MUX_DATA(0, i) <= MDR_OUT(i);
    R1_MUX_DATA(1, i) <= ALU_OUT(i);
    R1_MUX_DATA(2, i) <= R0_OUT(i);
    R1_MUX_DATA(3, i) <= '0';
```

```
end generate;
```

```
R1_MUX: lpm_mux
```

```
    generic map(lpm_width=> 8, lpm_size=> 4, lpm_widths=> 2)
```

```
    port map(data=>R1_MUX_DATA, result=>R1_MUX_OUT, sel=>R1_SEL);
```

```
REG1: lpm_ff
```

```
    generic map(lpm_width=>8)
```

```
    port map(enable=>R1_ENABLE, data=>R1_MUX_OUT, q=>R1_OUT,  
clock=>CLOCK);
```

```
STACK_POINTER: lpm_counter
```

```
    generic map(lpm_width=>8)
```

```
    port map(sload=>SP_LOAD, data=>MDR_OUT, q=>SP_OUT,  
cnt_en=>SP_ENABLE, updown=>SP_INC, clock=>CLOCK);
```

```
V_MUX_DATA(0, 0) <= V_MUX_0;
```

```
V_MUX_DATA(1, 0) <= V_MUX_1;
```

```
V_MUX: lpm_mux
```

```
    generic map(lpm_width=>1, lpm_size=>2, lpm_widths=>1)
```

```
    port map(data=>V_MUX_DATA, result=>V_MUX_OUT, sel=>V_MUX_SEL);
```

```
Z_MUX_DATA(0, 0) <= not V_MUX_OUT(0);
```

```
Z_MUX_DATA(1, 0) <= V_MUX_OUT(0);
```

```
Z_MUX: lpm_mux
```

```
    generic map(lpm_width=>1, lpm_size=>2, lpm_widths=>1)
```

```
    port map(data=>Z_MUX_DATA, result=>Z_MUX_OUT, sel=>Z_SEL);
```

```

    REG_Z: lpm_ff
        generic map(lpm_width=>1)
        port map(enable=>Z_LOAD, data=>Z_MUX_OUT, q=>Z_OUT,
clock=>CLOCK);

    Z_FLAG <= Z_OUT;

    R0Hi: seven_segment_display port map(digit=>R0_OUT(7 downto 4),
display=>R0SegHi);
    R0Lo: seven_segment_display port map(digit=>R0_OUT(3 downto 0),
display=>R0SegLo);
    R1Hi: seven_segment_display port map(digit=>R1_OUT(7 downto 4),
display=>R1SegHi);
    R1Lo: seven_segment_display port map(digit=>R1_OUT(3 downto 0),
display=>R1SegLo);
    pcHi: seven_segment_display port map(digit=>PC_OUT(7 downto 4),
display=>pcSegHi);
    pcLo: seven_segment_display port map(digit=>PC_OUT(3 downto 0),
display=>pcSegLo);
    spHi: seven_segment_display port map(digit=>SP_OUT(7 downto 4),
display=>spSegHi);
    spLo: seven_segment_display port map(digit=>SP_OUT(3 downto 0),
display=>spSegLo);

end structural;

```

- Register-Transfer Logic

Micro-operation Level RTL for CPU Instructions

```
# Develop the RTL statements for the CPU instructions:
```

All instructions **do** Instruction Fetch:

F1: $MAR \leftarrow PC$ # Load address of instruction

F2: $MDR \leftarrow M[MAR], PC \leftarrow PC + 1$ # Fetch instruction **and** increment PC

F3: $IR \leftarrow MDR$ # Decode instruction

nop **00000000**

- None -

loadi Rn, X **0001000n X**

LI1: $MAR \leftarrow PC$ # Load memory address of immediate operand

LI2: $MDR \leftarrow M[MAR], PC \leftarrow PC + 1$ # Fetch immediate operand **and** increment PC

LI3: $R0 \leftarrow MDR$ if $IR(0) = 0$, $R1 \leftarrow MDR$ if $IR(0) = 1$ # Load immediate value **into** **R0** if $IR(0) = 0$ else if $IR(0) = 1$ **into** **R1**

load Rn, X **0010000n X**

L1: $MAR \leftarrow PC$ # Load memory address of operand

L2: $MDR \leftarrow M[MAR], PC \leftarrow PC + 1$ # Fetch operand address **and** increment PC

L3: $MAR \leftarrow MDR$ # Load effective address

L4: $MDR \leftarrow M[MAR]$ # Fetch data from memory

L5: $R0 \leftarrow MDR$ if $IR(0) = 0$, $R1 \leftarrow MDR$ if $IR(0) = 1$ # Load data **into** **R0** if $IR(0) = 0$ else if $IR(0) = 1$ load **into** **R1**

store X, Rn **0011000n X**

ST1: $MAR \leftarrow PC$ # Load memory address of operand

ST2: $MDR \leftarrow M[MAR], PC \leftarrow PC + 1$ # Fetch operand address **and** increment PC

ST3: $MAR \leftarrow MDR$ # Load effective address

ST4: $MDR \leftarrow R0$ if $IR(0) = 0$, $MDR \leftarrow R1$ if $IR(0) = 1$ # Load data from **R0** if $IR(0) = 0$ else if $IR(0) = 1$ load from **R1**

ST5: $M[MAR] \leftarrow MDR$ # Store data **into** memory

move Rn, Rm 0100000n m!=n

M1: $R0 \leftarrow R1$ if $IR(0) = 0$, $R1 \leftarrow R0$ if $IR(0) = 1$ # Move value from R1 to R0 if $IR(0) = 0$
else if $IR(0) = 1$ move from R0 to R1

add Rn, Rm 0101000n m!=n

A1: $R0 \leftarrow R0 + R1$ if $IR(0) = 0$, $R1 \leftarrow R0 + R1$ if $IR(0) = 1$ # R0 plus R1 if $IR(0) = 0$ else if
 $IR(0) = 1$ R1 plus R0

sub Rn, Rm 0110000n m!=n

S1: $R0 \leftarrow R0 - R1$ if $IR(0) = 0$, $R1 \leftarrow R1 - R0$ if $IR(0) = 1$ # R0 minus R1 if $IR(0) = 0$ else if
 $IR(0) = 1$ R1 minus R0

testnz Rn 0111000n

TN1: $Z \leftarrow \text{NOT}(R0(0) \text{ OR } \dots \text{ OR } R0(7))$ if $IR(0) = 0$, $\leftarrow \text{NOT}(R1(0) \text{ OR } \dots \text{ OR } R1(7))$ if $IR(0)$
 $= 1$ # $Z = 1$ if R0 or R1 is nonzero

testz Rn 1000000n

T1: $Z \leftarrow R0(0) \text{ OR } \dots \text{ OR } R0(7)$ if $IR(0) = 0$, $\leftarrow R1(0) \text{ OR } \dots \text{ OR } R1(7)$ if $IR(0) = 1$ # $Z = 1$ if
R0 or R1 is nonzero

jump X 10010000 X

J1: $MAR \leftarrow PC$ # Load memory address of jump target

J2: $MDR \leftarrow M[MAR]$ # Fetch jump target address

J3: $PC \leftarrow MDR$ # Jump to target address

jumpz X 10100000 X

JZ1: $MAR \leftarrow PC$ # Load memory address of jump target

JZ2: $MDR \leftarrow M[MAR]$, $PC \leftarrow PC + 1$ # Fetch jump target address and increment PC

JZ3: $PC \leftarrow MDR$ if $Z=1$ # Jump if Z flag is set

loadsp X 10110000 X

LS1: MAR \leftarrow PC # Load memory address of operand

LS2: MDR \leftarrow M[MAR], PC \leftarrow PC + 1 # Fetch operand and increment PC

LS3: SP \leftarrow MDR # Load operand into SP

peek Rn 1100000n

P1: MAR \leftarrow SP # Load address from stack pointer

P2: MDR \leftarrow M[MAR] # Fetch value from stack

P3: R0 \leftarrow MDR if IR(0) = 0, R1 \leftarrow MDR if IR(0) = 1 # Peek value from stack into R0 if
IR(0) = 0 else if IR(0) = 1 into R1

push Rn 1101000n

PU1: SP \leftarrow SP - 1 # Decrement stack pointer

PU2: MAR \leftarrow SP # Load address from stack pointer

PU3: MDR \leftarrow R0 if IR(0) = 0, MDR \leftarrow R1 if IR(0) = 1 # Load value from R0 if IR(0) = 0
else if IR(0) = 1 from R1

PU4: M[MAR] \leftarrow MDR # Push value onto stack

pop Rn 1110000n

PO1: MAR \leftarrow SP # Load address from stack pointer

PO2: MDR \leftarrow M[MAR] # Fetch value from stack

PO3: R0 \leftarrow MDR if IR(0) = 0, R1 \leftarrow MDR if IR(0) = 1 # Load value into R0 if IR(0) = 0 else
if IR(0) = 1 into R1

PO4: SP \leftarrow SP + 1 # Increment stack pointer

halt 11110000

H1: PC \leftarrow 0 # Stop execution by resetting PC

- Pin Assignments

Pin Assignments for testing the Microsequencer without a PC Register

Node Name	Direction	Location
addr_hex0_disp0[0]	Output	PIN_G18
addr_hex0_disp0[1]	Output	PIN_F22
addr_hex0_disp0[2]	Output	PIN_E17
addr_hex0_disp0[3]	Output	PIN_L26
addr_hex0_disp0[4]	Output	PIN_L25
addr_hex0_disp0[5]	Output	PIN_J22
addr_hex0_disp0[6]	Output	PIN_H22
addr_hex1_disp1[0]	Output	PIN_M24
addr_hex1_disp1[1]	Output	PIN_Y22
addr_hex1_disp1[2]	Output	PIN_W21
addr_hex1_disp1[3]	Output	PIN_W22
addr_hex1_disp1[4]	Output	PIN_W25
addr_hex1_disp1[5]	Output	PIN_U23
addr_hex1_disp1[6]	Output	PIN_U24
button	Input	PIN_R24
clear	Input	PIN_AB28
ctrlSignals[0]	Output	PIN_H19
ctrlSignals[1]	Output	PIN_J19
ctrlSignals[2]	Output	PIN_E18
ctrlSignals[3]	Output	PIN_F18
ctrlSignals[4]	Output	PIN_F21
ctrlSignals[5]	Output	PIN_E19
ctrlSignals[6]	Output	PIN_F19
ctrlSignals[7]	Output	PIN_G19
M_disp[0]	Output	PIN_AA25
M_disp[1]	Output	PIN_AA26
M_disp[2]	Output	PIN_Y25
M_disp[3]	Output	PIN_W26
M_disp[4]	Output	PIN_Y26
M_disp[5]	Output	PIN_W27
M_disp[6]	Output	PIN_W28
useqEnOut	Output	PIN_H15

Pin Assignments for testing the Microsequencer with a PC Register

Node Name	Direction	Location
addr_hex0_disp0[0]	Output	PIN_G18
addr_hex0_disp0[1]	Output	PIN_F22
addr_hex0_disp0[2]	Output	PIN_E17
addr_hex0_disp0[3]	Output	PIN_L26
addr_hex0_disp0[4]	Output	PIN_L25
addr_hex0_disp0[5]	Output	PIN_J22
addr_hex0_disp0[6]	Output	PIN_H22
addr_hex1_disp1[0]	Output	PIN_M24
addr_hex1_disp1[1]	Output	PIN_Y22
addr_hex1_disp1[2]	Output	PIN_W21
addr_hex1_disp1[3]	Output	PIN_W22
addr_hex1_disp1[4]	Output	PIN_W25
addr_hex1_disp1[5]	Output	PIN_U23
addr_hex1_disp1[6]	Output	PIN_U24
button	Input	PIN_R24
clear	Input	PIN_AB28
ctrlSignals[0]	Output	PIN_H19
ctrlSignals[1]	Output	PIN_J19
ctrlSignals[2]	Output	PIN_E18
ctrlSignals[3]	Output	PIN_F18
ctrlSignals[4]	Output	PIN_F21
ctrlSignals[5]	Output	PIN_E19
ctrlSignals[6]	Output	PIN_F19
ctrlSignals[7]	Output	PIN_G19
M_disp[0]	Output	PIN_AA25
M_disp[1]	Output	PIN_AA26
M_disp[2]	Output	PIN_Y25
M_disp[3]	Output	PIN_W26
M_disp[4]	Output	PIN_Y26
M_disp[5]	Output	PIN_W27
M_disp[6]	Output	PIN_W28
pc_Seq0[0]	Output	PIN_AB19
pc_Seq0[1]	Output	PIN_AA19
pc_Seq0[2]	Output	PIN_AG21
pc_Seq0[3]	Output	PIN_AH21
pc_Seq0[4]	Output	PIN_AE19
pc_Seq0[5]	Output	PIN_AF19
pc_Seq0[6]	Output	PIN_AE18
pc_Seq1[0]	Output	PIN_AD18
pc_Seq1[1]	Output	PIN_AC18
pc_Seq1[2]	Output	PIN_AB18
pc_Seq1[3]	Output	PIN_AH19
pc_Seq1[4]	Output	PIN_AG19
pc_Seq1[5]	Output	PIN_AF18
pc_Seq1[6]	Output	PIN_AH18
useqEnOut	Output	PIN_H15

Pin Assignments for reading and writing to/from RAM using a Microsequencer

Node Name	Direction	Location
clear	Input	PIN_AB28
ctrlSignals[0]	Output	PIN_H19
ctrlSignals[1]	Output	PIN_J19
ctrlSignals[2]	Output	PIN_E18
ctrlSignals[3]	Output	PIN_F18
ctrlSignals[4]	Output	PIN_F21
ctrlSignals[5]	Output	PIN_E19
ctrlSignals[6]	Output	PIN_F19
ctrlSignals[7]	Output	PIN_G19
marData[7]	Input	PIN_Y23
marData[6]	Input	PIN_Y24
marData[5]	Input	PIN_AA22
marData[4]	Input	PIN_AA23
marData[3]	Input	PIN_AA24
marData[2]	Input	PIN_AB23
marData[1]	Input	PIN_AB24
marData[0]	Input	PIN_AC24
marSeqHi[0]	Output	PIN_M24
marSeqHi[1]	Output	PIN_Y22
marSeqHi[2]	Output	PIN_W21
marSeqHi[3]	Output	PIN_W22
marSeqHi[4]	Output	PIN_W25
marSeqHi[5]	Output	PIN_U23
marSeqHi[6]	Output	PIN_U24
marSeqLo[0]	Output	PIN_G18
marSeqLo[1]	Output	PIN_F22
marSeqLo[2]	Output	PIN_E17
marSeqLo[3]	Output	PIN_L26
marSeqLo[4]	Output	PIN_L25
marSeqLo[5]	Output	PIN_J22
marSeqLo[6]	Output	PIN_H22
mdrSeqHi[0]	Output	PIN_V21
mdrSeqHi[1]	Output	PIN_U21
mdrSeqHi[2]	Output	PIN_AB20
mdrSeqHi[3]	Output	PIN_AA21
mdrSeqHi[4]	Output	PIN_AD24
mdrSeqHi[5]	Output	PIN_AF23
mdrSeqHi[6]	Output	PIN_Y19
mdrSeqLo[0]	Output	PIN_AA25
mdrSeqLo[1]	Output	PIN_AA26
mdrSeqLo[2]	Output	PIN_Y25
mdrSeqLo[3]	Output	PIN_W26
mdrSeqLo[4]	Output	PIN_Y26
mdrSeqLo[5]	Output	PIN_W27
mdrSeqLo[6]	Output	PIN_W28
nextAddrHi[0]	Output	PIN_AD18
nextAddrHi[1]	Output	PIN_AC18
nextAddrHi[2]	Output	PIN_AB18
nextAddrHi[3]	Output	PIN_AH19
nextAddrHi[4]	Output	PIN_AG19
nextAddrHi[5]	Output	PIN_AF18
nextAddrHi[6]	Output	PIN_AH18
nextAddrLo[0]	Output	PIN_AB19
nextAddrLo[1]	Output	PIN_AA19
nextAddrLo[2]	Output	PIN_AG21
nextAddrLo[3]	Output	PIN_AH21
nextAddrLo[4]	Output	PIN_AE19
nextAddrLo[5]	Output	PIN_AF19
nextAddrLo[6]	Output	PIN_AE18
useqEnOut	Output	PIN_H15

Pin assignments for the Microsequencer-based CPU implementation

	Node Name	Direction	Location
in	button	Input	PIN_M21
in	clear	Input	PIN_Y23
out	R0SeqHi[0]	Output	PIN_M24
out	R0SeqHi[1]	Output	PIN_Y22
out	R0SeqHi[2]	Output	PIN_W21
out	R0SeqHi[3]	Output	PIN_W22
out	R0SeqHi[4]	Output	PIN_W25
out	R0SeqHi[5]	Output	PIN_U23
out	R0SeqHi[6]	Output	PIN_U24
out	R0SeqLo[0]	Output	PIN_G18
out	R0SeqLo[1]	Output	PIN_F22
out	R0SeqLo[2]	Output	PIN_E17
out	R0SeqLo[3]	Output	PIN_L26
out	R0SeqLo[4]	Output	PIN_L25
out	R0SeqLo[5]	Output	PIN_J22
out	R0SeqLo[6]	Output	PIN_H22
out	R1SeqHi[0]	Output	PIN_V21
out	R1SeqHi[1]	Output	PIN_U21
out	R1SeqHi[2]	Output	PIN_AB20
out	R1SeqHi[3]	Output	PIN_AA21
out	R1SeqHi[4]	Output	PIN_AD24
out	R1SeqHi[5]	Output	PIN_AF23
out	R1SeqHi[6]	Output	PIN_Y19
out	R1SeqLo[0]	Output	PIN_AA25
out	R1SeqLo[1]	Output	PIN_AA26
out	R1SeqLo[2]	Output	PIN_Y25
out	R1SeqLo[3]	Output	PIN_W26
out	R1SeqLo[4]	Output	PIN_Y26
out	R1SeqLo[5]	Output	PIN_W27
out	R1SeqLo[6]	Output	PIN_W28
out	Z_FLAG[0]	Output	PIN_H15
out	pcSeqHi[0]	Output	PIN_AD18
out	pcSeqHi[1]	Output	PIN_AC18
out	pcSeqHi[2]	Output	PIN_AB18
out	pcSeqHi[3]	Output	PIN_AH19
out	pcSeqHi[4]	Output	PIN_AG19
out	pcSeqHi[5]	Output	PIN_AF18
out	pcSeqHi[6]	Output	PIN_AH18
out	pcSeqLo[0]	Output	PIN_AB19
out	pcSeqLo[1]	Output	PIN_AA19
out	pcSeqLo[2]	Output	PIN_AG21
out	pcSeqLo[3]	Output	PIN_AH21
out	pcSeqLo[4]	Output	PIN_AE19
out	pcSeqLo[5]	Output	PIN_AF19
out	pcSeqLo[6]	Output	PIN_AE18
out	spSeqHi[0]	Output	PIN_AD17
out	spSeqHi[1]	Output	PIN_AE17
out	spSeqHi[2]	Output	PIN_AG17
out	spSeqHi[3]	Output	PIN_AH17
out	spSeqHi[4]	Output	PIN_AF17
out	spSeqHi[5]	Output	PIN_AG18
out	spSeqHi[6]	Output	PIN_AA14
out	spSeqLo[0]	Output	PIN_AA17
out	spSeqLo[1]	Output	PIN_AB16
out	spSeqLo[2]	Output	PIN_AA16
out	spSeqLo[3]	Output	PIN_AB17
out	spSeqLo[4]	Output	PIN_AB15
out	spSeqLo[5]	Output	PIN_AA15
out	spSeqLo[6]	Output	PIN_AC17

- Memory Initialization Files

Memory Initialization File for testing the Microsequencer without a PC Register

```

1  -- uROM Test File
2  -- 8-bit control signals
3  WIDTH=17;
4  DEPTH=256;
5  ADDRESS_RADIX=HEX;
6  DATA_RADIX=BIN;
7  CONTENT BEGIN
8    [0..FF]: 000000000000000000;
9  --    uop
10 --    01234567M01234567
11  00: 000000000000000001; -- control signal = 00000000, next address = 0x01
12  01: 00000001000000010; -- control signal = 00000001, next address = 0x02
13  02: 00000010000000011; -- control signal = 00000010, next address = 0x03
14  03: 00000011000000100; -- control signal = 00000011, next address = 0x04
15  04: 00000100100000000; -- control signal = 00000100, use MAP, go to address 0x30
16  30: 00000101000110001; -- control signal = 00000101, next address = 0x31
17  31: 00000110000110010; -- control signal = 00000110, next address = 0x32
18  32: 00000111000110011; -- control signal = 00000111, next address = 0x33
19  33: 00001000000000001; -- control signal = 00001000, next address = 0x01
20  END;
```

Memory Initialization File for testing the Microsequencer with a PC Register

```

1  -- uROM Test File
2  -- 8-bit control signals
3  WIDTH=17;
4  DEPTH=256;
5  ADDRESS_RADIX=HEX;
6  DATA_RADIX=BIN;
7  CONTENT BEGIN
8    [0..FF]: 000000000000000000;
9  --    uop
10 --    01234567M01234567
11  00: 000000000000000001; -- control signal = 00000000, next address = 0x01
12  01: 00100001000000010; -- control signal = 00100001, next address = 0x02, clear PC, PC = 0x00
13  02: 10000010000000011; -- control signal = 10000010, next address = 0x03, inc PC, PC = 0x01
14  03: 10000011000000100; -- control signal = 10000011, next address = 0x04, inc PC, PC = 0x02
15  04: 00000100100000000; -- control signal = 00000100, use MAP, go to address 0x30
16  30: 01000101000110001; -- control signal = 01000101, next address = 0x31, load PC, PC = 0xAA
17  31: 00000110000110010; -- control signal = 00000110, next address = 0x32
18  32: 10000111000110011; -- control signal = 10000111, next address = 0x33, inc PC, PC = 0xAB
19  33: 00001000000000001; -- control signal = 00001000, next address = 0x01,
20  END;
```

Memory Initialization Files for reading and writing to/from RAM using a Microsequencer

```
1  -- uROM Test File
2  -- 8-bit control signals
3
4  WIDTH=17;
5  DEPTH=256;
6  ADDRESS_RADIX=HEX;
7  DATA_RADIX=BIN;
8
9  CONTENT BEGIN
10     [0..FF]: 000000000000000000;
11     --      uop
12     --      01234567M01234567
13     00: 0000000000000000001; -- control signal (cs) = 00000000, next address (na) = 0x01
14     01: 100000010000000010; -- cs = 10000001, na = 0x02, Load MAR from sw, MAR = 0x54
15     02: 010000100000000011; -- cs = 01000010, na = 0x03, MDR <- M[MAR], MDR = 0xFC
16     03: 100000110000000100; -- cs = 10000011, na = 0x04, Load MAR from sw, MAR = 0x55
17     04: 010001000000000101; -- cs = 01000100, na = 0x05, MDR <- M[MAR], MDR = 0xDD
18     05: 100001010000000110; -- cs = 10000101, na = 0x06, Load MAR from sw, MAR = 0x56
19     06: 001001100000000111; -- cs = 00100110, na = 0x07, M[MAR] <- MDR
20     07: 10000111000001000; -- cs = 10000111, na = 0x08, Load MAR from sw, MAR = 0x54
21     08: 01001000000001001; -- cs = 01001000, na = 0x09, MDR <- M[MAR], MDR = 0xFC
22     09: 10001001000001010; -- cs = 10001001, na = 0x0A, Load MAR from sw, MAR = 0x56
23     0A: 01001010000000000; -- cs = 01001010, na = 0x00, MDR <- M[MAR], MDR = 0xDD
24  END;
```



```
1  -- RAM Test File
2
3  WIDTH=8;
4  DEPTH=256;
5  ADDRESS_RADIX=HEX;
6  DATA_RADIX=HEX;
7
8  CONTENT BEGIN
9     [0..FF]: 0;
10     54: FC;
11     55: DD;
12     56: AA;
13  END;
```

Memory Initialization Files for the ROM of the Microsequencer inside of our CPU

```
1 WIDTH=33;
2 DEPTH=256;
3
4 ADDRESS_RADIX=HEX;
5 DATA_RADIX=BIN;
6
7 -- Current Address: UOP(1-24)MAP(8)NEXTADDRESS(7-0)
8 -- 0xADDRESS: 123456789(10) (11) (12) (13) (14) (15) (16) (17) (18) (19) (20) (21) (22) (23) (24) 876543210
9
10 CONTENT BEGIN
11 [0..FF]: 00000000000000000000000000000000;
12 00: 00000000000000000000000000000001;
13 01: 00000010000000000000000000000010;
14 02: 01000000100000000000000000000011;
15 03: 001000000000000000000000010000001;
16 10: 000000100000000000000000000010001;
17 11: 010000001000000000000000000010010;
18 12: 00000000000100100000000000000001;
19 20: 000000100000000000000000000010001;
20 21: 010000001000000000000000000010010;
21 22: 000001100000000000000000000010011;
22 23: 0000000010000000000000000000100100;
23 24: 00000000000100100000000000000001;
24 30: 0000001000000000000000000000110001;
25 31: 0100000010000000000000000000110010;
26 32: 0001011000000000000000000000110011;
27 33: 0000000110000000000000000000110100;
28 34: 00010000000000000000000000000001;
29 40: 00000000010110100000000000000001;
30 50: 00000000001101110000000000000001;
31 60: 00000000001101100000000000000001;
32 70: 00000000000000001010000000000001;
33 80: 00000000000000001110000000000001;
34 90: 00000010000000000000000010010001;
35 91: 00000000100000000000000001001001;
36 92: 00000000000000000001000000000001;
37 A0: 000000100000000000000000010100001;
38 A1: 010000001000000000000000010100010;
39 A2: 00000000000000000000100000000001;
40 B0: 000000100000000000000000010110001;
41 B1: 010000001000000000000000010110010;
42 B2: 00000000000000000000100000000001;
43 C0: 000010100000000000000000011000001;
44 C1: 000000001000000000000000011000010;
00: 00000000000000000000000000000001;
01: 00000010000000000000000000000010;
02: 01000000100000000000000000000011;
03: 001000000000000000000000010000001;
10: 000000100000000000000000000010001;
11: 010000001000000000000000000010010;
12: 00000000000100100000000000000001;
20: 000000100000000000000000000010001;
21: 010000001000000000000000000010010;
22: 000001100000000000000000000010011;
23: 0000000010000000000000000000100100;
24: 00000000000100100000000000000001;
30: 0000001000000000000000000000110001;
31: 0100000010000000000000000000110010;
32: 0001011000000000000000000000110011;
33: 0000000110000000000000000000110100;
34: 00010000000000000000000000000001;
40: 00000000010110100000000000000001;
50: 00000000001101110000000000000001;
60: 00000000001101100000000000000001;
70: 00000000000000001010000000000001;
80: 00000000000000001110000000000001;
90: 000000100000000000000000010010001;
91: 00000000100000000000000001001001;
92: 00000000000000000001000000000001;
A0: 000000100000000000000000010100001;
A1: 010000001000000000000000010100010;
A2: 00000000000000000000100000000001;
B0: 000000100000000000000000010110001;
B1: 010000001000000000000000010110010;
B2: 00000000000000000000100000000001;
C0: 000010100000000000000000011000001;
C1: 000000001000000000000000011000010;
END;
```


ram_files

- Tables

CPU Instructions

Instruction	Instruction code	Operation
NOP	00000000	No operation
LOADI Rn,X	0001000n X	$R_n \leftarrow X$
LOAD Rn,X	0010000n X	$R_n \leftarrow M[X]$
STORE X,Rm	0011000m X	$M[X] \leftarrow R_m$
MOVE Rn,Rm	0100000n	$R_n \leftarrow R_m, m \neq n$
ADD Rn,Rm	0101000n	$R_n \leftarrow R_n + R_m, m \neq n$
SUB Rn,Rm	0110000n	$R_n \leftarrow R_n - R_m, m \neq n$
TESTNZ Rm	0111000m	$Z \leftarrow \text{not } V, V = \text{OR of the bits of } R_m$
TESTZ Rm	1000000m	$Z \leftarrow V, V = \text{OR of the bits of } R_m$
JUMP X	10010000 X	$PC \leftarrow X$
JUMPZ X	10100000 X	If $(Z = 1)$ then $PC \leftarrow X$
LOADSP X	10110000 X	$SP \leftarrow X$
PEEP Rn	1100000n	$R_n \leftarrow M[SP]$
PUSH Rn	1101000n	$M[--SP] \leftarrow R_n$ Pre-increment
POP Rn	1110000n	$R_n \leftarrow M[SP++]$ Post-decrement
HALT	11110000	$PC \leftarrow 0$, stop microsequencer

ROM Output

 

- Spreadsheets

[+ Microsequencer ROM](#)

[+ FPGA Pin Layout](#)