


# Experiment 7

- Microprogrammed CPU Design
- Implement with VHDL using lpm components and structural modeling
- Multi-week

# Microprogrammed CPU

- Review Chapter 7 of Carpinelli's Computer Systems Organization & Architecture
- The entire CPU including RAM will be implemented with the DE2
- The VHDL code for the micro sequencer is provided

# Overall Block Diagram

 

reset – set PC to 0

# CPU Organization

- Program Counter (PC) – 8 bits
- Memory Address Register (MAR) – 8 bits
- Instruction Register (IR) – 8 bits
- Memory Data Register (MDR) – 8 bits
- Register File (R0-R1) – 8 bits
- Condition flip-flop (Z) – 1 bit
- Stack Pointer (SP) – 8 bits

# CPU Instruction (Fall 2025)

Instruction	Instruction code	Operation
NOP	00000000	No operation
LOADI R <sub>n</sub> ,X	0001000n X	$R_n \leftarrow X$
LOAD R <sub>n</sub> ,X	0010000n X	$R_n \leftarrow M[X]$
STORE X,R <sub>m</sub>	0011000m X	$M[X] \leftarrow R_m$
MOVE R <sub>n</sub> ,R <sub>m</sub>	0100000n	$R_n \leftarrow R_m, m \neq n$
ADD R <sub>n</sub> ,R <sub>m</sub>	0101000n	$R_n \leftarrow R_n + R_m, m \neq n$
SUB R <sub>n</sub> ,R <sub>m</sub>	0110000n	$R_n \leftarrow R_n - R_m, m \neq n$
TESTNZ R <sub>m</sub>	0111000m	$Z \leftarrow \text{not } V, V = \text{OR of the bits of } R_m$
TESTZ R <sub>m</sub>	1000000m	$Z \leftarrow V, V = \text{OR of the bits of } R_m$
JUMP X	10010000 X	$PC \leftarrow X$
JUMPZ X	10100000 X	If (Z = 1) then $PC \leftarrow X$
LOADSP X	10110000 X	$SP \leftarrow X$
PEEP R <sub>n</sub>	1100000n	$R_n \leftarrow M[SP]$
PUSH R <sub>n</sub>	1101000n	$M[--SP] \leftarrow R_n$ Pre-decrement
POP R <sub>n</sub>	1110000n	$R_n \leftarrow M[SP++]$ Post-increment
HALT	11110000	$PC \leftarrow 0$ , stop microsequencer

X = 8-bit data or  
address  
m, n = 0 or 1, m ≠ n

Mnemonic	Code (Binary)	Code (HEX)
nop	00000000	00
loadi R0,FF	00010000 11111111	10 FF
loadi R1,FF	00010001 11111111	11 FF
load R0,FF	00100000 11111111	20 FF
load R1,FF	00100001 11111111	21 FF
store FF,R0	00110000 11111111	30 FF
store FF,R1	00110001 11111111	31 FF
addi r0,FF	01000000 11111111	40 FF
addi r1,FF	01000001 11111111	41 FF
add R0,R1	01010000	50
add R1,R0	01010001	51
sub R0,R1	01100000	60
sub R1,R0	01100001	61

Mnemonic	Code (Binary)	Code (Hex)
testnz R0	01110000	70
testnz R1	01110001	71
testz R0	10000000	80
testz R1	10000001	81
jump FF	10010000 11111111	90 FF
jumpz FF	10100000 11111111	A0 FF
loadsp FF	10110000 11111111	B0 FF
peep R0	11000000	C0
peep R1	11000001	C1
push R0	11010000	D0
push R1	11010001	D1
pop R0	11100000	E0
pop R1	11100001	E1
halt	11110000	F0

# Instruction Format

- Instructions can be 1 byte or 2 bytes
- Sixteen instructions
- 1<sup>st</sup> byte is opcode
- If present, 2<sup>nd</sup> byte is address or data





# Components

- Custom Microsequencer is provided
  - The VHDL code are posted on Canvas.
- Use `lpm_counter` for PC, SP so you can also perform load and increment
- Use `lpm_ff` for other registers
- You can use VHDL statements for simple stuffs
 
# Microsequencer

- Clock - system clock
- Enable - enables microsequencer
- Clear - reset the address register in the microsequencer to 0
- Opcode - 4-bit
- Requires two clock cycles




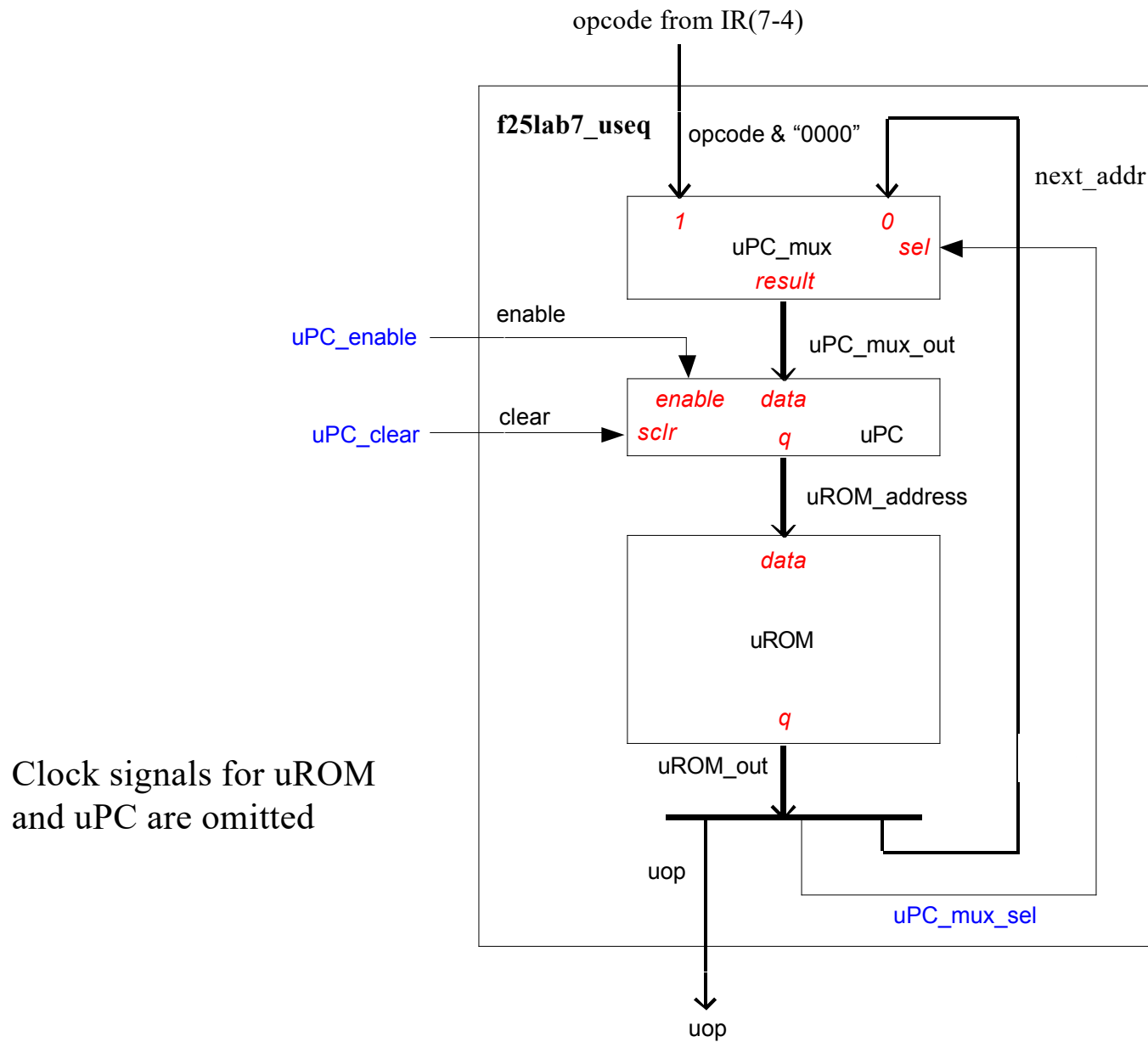

# Micro-ROM


- 256 words
- Width of each micro-ROM word is `uROM_width`
- `uROM_file` is the name of the mif with the content of the micro-ROM

# Micro-ROM format

 
 
# Component Declaration


```
component f25lab7_useq
generic (uROM_width: integer;
         uROM_file: string);
port (opcode: in std_logic_vector(3 downto 0);
       uop: out std_logic_vector(1 to (uROM_width-9));
       debug_map_addr: out std_logic_vector(8 downto 0); -- for debugging
       enable, clear, clock: in std_logic);
end component;
```



# Displaying Results

- Display the content of R0, R1
- Display the content of PC
- Display the content of SP
- Addition display of other registers maybe needed for debugging.
- You can use seven segment or LCD for display

# RAM Connection

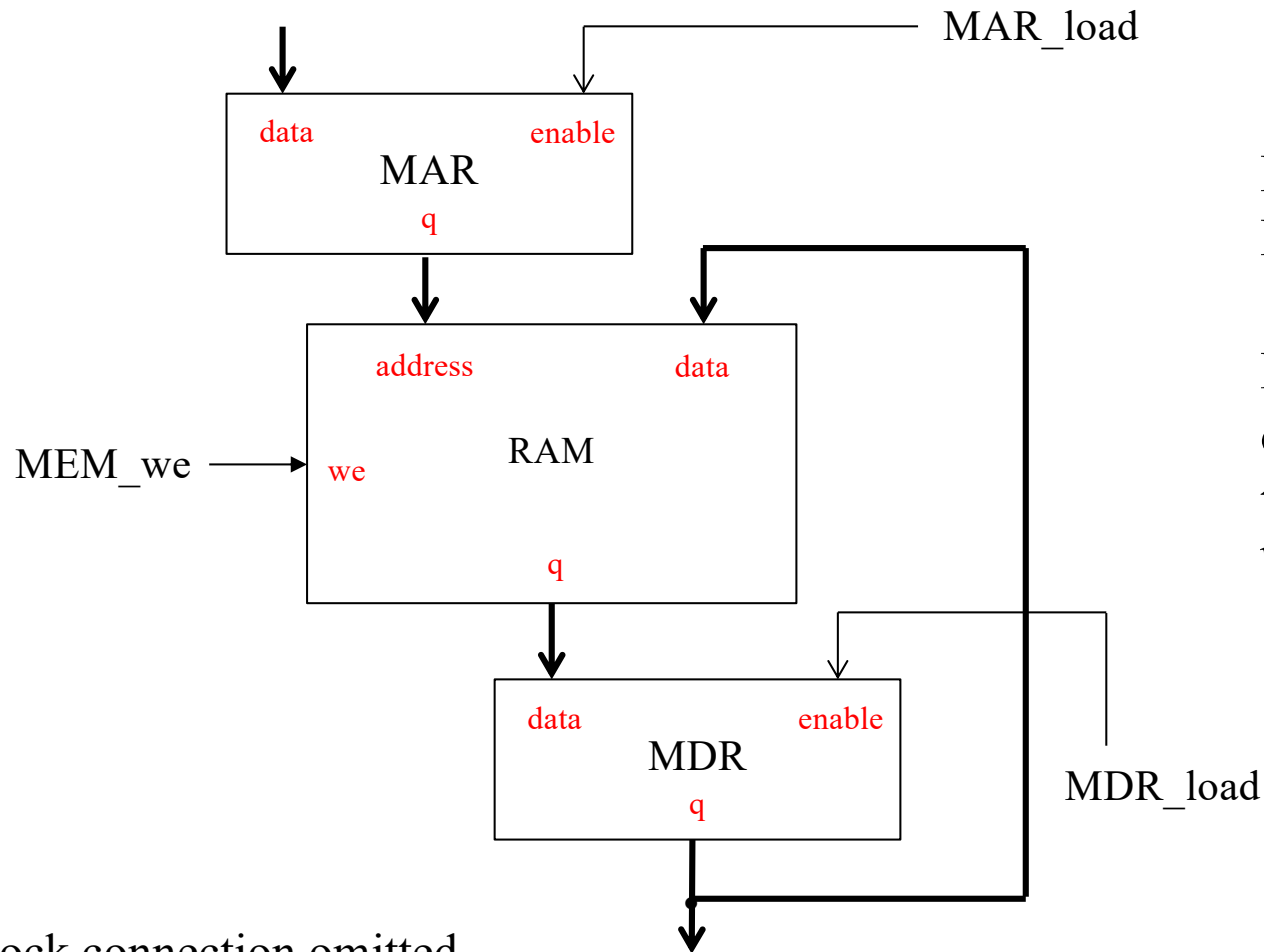

$MAR \leftarrow \text{address}$   
 $MDR \leftarrow M[MAR]$

Memory will always  
output the content of  
the location indicated  
by the address port

Clock connection omitted



# Register Transfer Language

- RTL is a level of abstraction that describes how data flows between registers in a digital circuit.

destination  $\leftarrow$  source

# Instruction Fetch

1. Move address in PC to MAR
2. Read instruction from memory and store it in MDR, increment PC
3. Move instruction from MDR to IR
4. Decode opcode in IR (done by mapping in the microsequencer)

# Register Transfer Language

- Instruction Fetch
  1.  $MAR \leftarrow PC$
  2.  $MDR \leftarrow M[MAR], PC \leftarrow PC+1$
  3.  $IR \leftarrow MDR$

Each line corresponds to a microinstruction

# LOAD $R_n, X \quad R_n \leftarrow M[X]$

IF1:  $MAR \leftarrow PC$

IF2:  $MDR \leftarrow M[MAR], PC \leftarrow PC+1$

IF3:  $IR \leftarrow MDR$

LOAD1:  $MAR \leftarrow PC$


LOAD2:  $MDR \leftarrow M[MAR], PC \leftarrow PC+1$

LOAD3:  $MAR \leftarrow MDR$

LOAD4:  $MDR \leftarrow M[MAR]$

LOAD5:  $R0 \leftarrow MDR$  if  $IR(0) = 0$ ,  $R1 \leftarrow MDR$  if  $IR(0) = 1$

 LOAD  $R1, C5 = 21 \quad C5$   
= 00100001 11000101




# LOAD R1,C5
 
# R1 = FF

IF1: MAR  $\leftarrow$  PC

IF2: MDR  $\leftarrow$  M[MAR], PC  $\leftarrow$  PC+1



PC	12
MAR	--
MR	--
IR	--
R1	--

PC	12
MAR	12
MDR	--
IR	--
R1	--

PC	13
MAR	12
MDR	21
IR	--
R1	--

IF3: IR  $\leftarrow$  MDR

LOAD1: MAR  $\leftarrow$  PC

LOAD2: MDR  $\leftarrow$  M[MAR], PC  $\leftarrow$  PC+1

LOAD3: MAR  $\leftarrow$  MDR

PC	13
MAR	12
MDR	21
IR	21
R1	--

PC	13
MAR	13
MDR	21
IR	21
R1	--

PC	14
MAR	13
MDR	C5
IR	21
R1	--

PC	14
MAR	C5
MDR	C5
IR	21
R1	--

LOAD2: MDR  $\leftarrow$  M[MAR]

LOAD5: R1  $\leftarrow$  MDR if IR(0) = 1

PC	14
MAR	C5
MDR	FF
IR	21
R1	--

PC	14
MAR	C5
MDR	FF
IR	21
R1	FF

IF1: MAR  $\leftarrow$  PC  
 IF2: MDR  $\leftarrow$  M[MAR], PC  $\leftarrow$  PC+1  
 IF3: IR  $\leftarrow$  MDR  
 LOAD1: MAR  $\leftarrow$  PC  
 LOAD2: MDR  $\leftarrow$  M[MAR], PC  $\leftarrow$  PC+1  
 LOAD3: MAR  $\leftarrow$  MDR  
 LOAD4: MDR  $\leftarrow$  M[MAR]  
 LOAD5: R0  $\leftarrow$  MDR if IR(0) = 0, R1  $\leftarrow$  MDR if IR(0) = 1